

CHAPTER-2

Introduction:

material - Depending upon the conductivity of materials are divided into 3 types-

↳ conductor

↳ semiconductor

↳ insulator

conductor - conductivity of a conductor is very high.

Ex: Iron, Aluminium.


Insulator - conductivity of insulators is very poor.

Ex: wood, glass


semiconductor - conductivity of semiconductors lies between conductors and insulators.

Ex: Si, Ge, As, GaAs, LED (Light emitting diode)

Energy band of conductor:

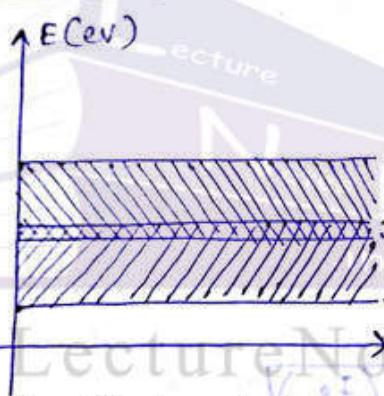


Energy band of insulator:

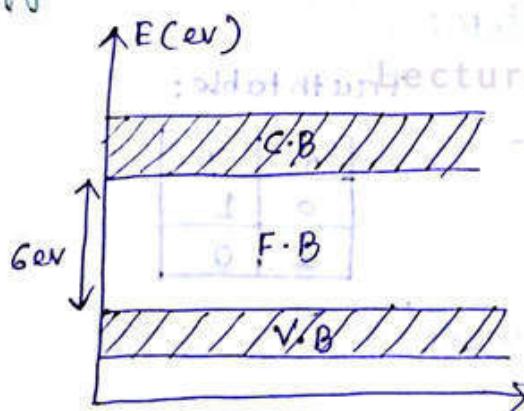

C.B. → conduction band
 V.B. → valence band
 F.B. → forbidden energy gap

Energy band of Semiconductor:

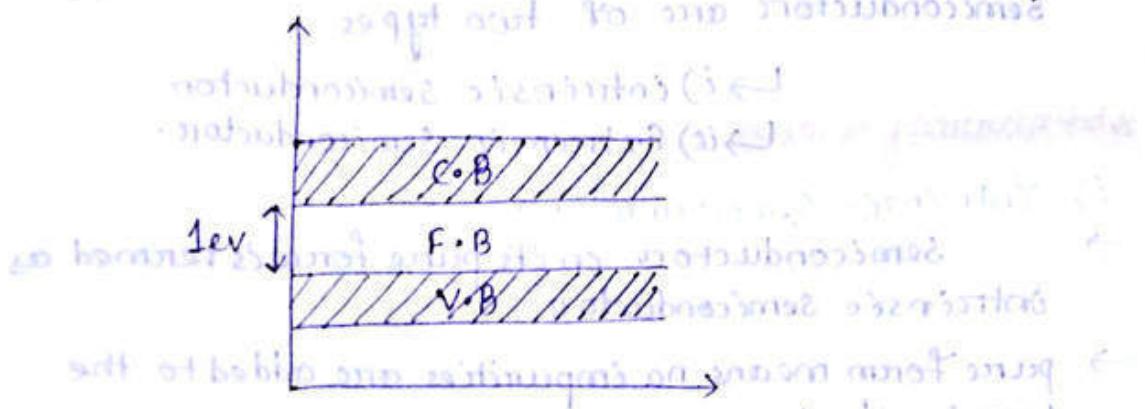


Band theory:

- Every material has some small range of allowed band of energies where e^-s can move freely.
- There may be more than one allowed band such as valence band, conduction band.
- There are some regions which are not occupied by energy levels. These regions are called forbidden band.
- No e^-s can stay in forbidden band.
- The measure of energy level is called ev.
- Width of the forbidden band determines whether the material is conductor, insulator or semiconductor.

Assignment:

$$v(t) = \frac{V_m}{2} + \frac{V_m}{\pi} \left[\frac{1}{2} \sin 200\omega t + \frac{1}{3} \sin 400\omega t + \frac{1}{4} \sin 600\omega t + \dots \right]$$

→

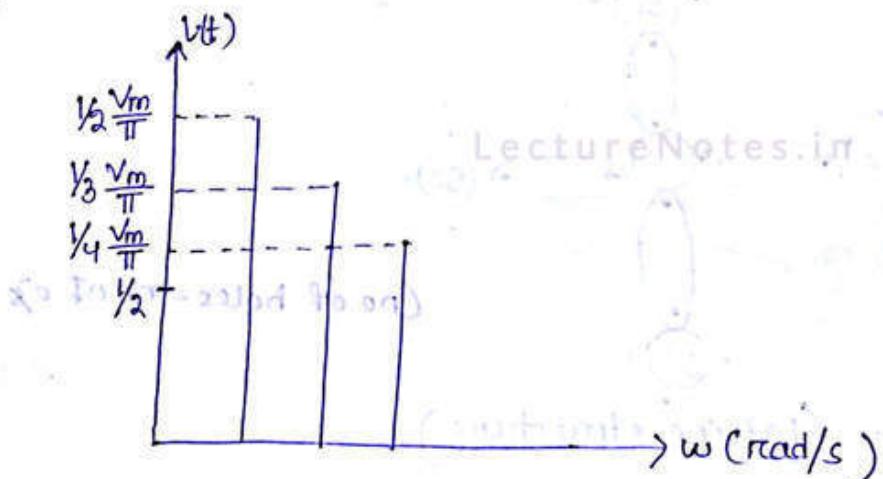

Semiconductor:

Semiconductor are of two types

- ↳ i) Intrinsic Semiconductor.
- ↳ ii) Extrinsic Semiconductor.

i) Intrinsic Semiconductor:

- Semiconductor in its pure form is termed as intrinsic semiconductor.
- pure form means no impurities are added to the semiconductor.

ii) Extrinsic Semiconductor:


- If any impurity is added to pure form of semiconductor then that is called extrinsic semiconductor.
- Extrinsic Semiconductor are of two types. i.e.


↳ a) p-type Semiconductor.

↳ b) N-type Semiconductor.

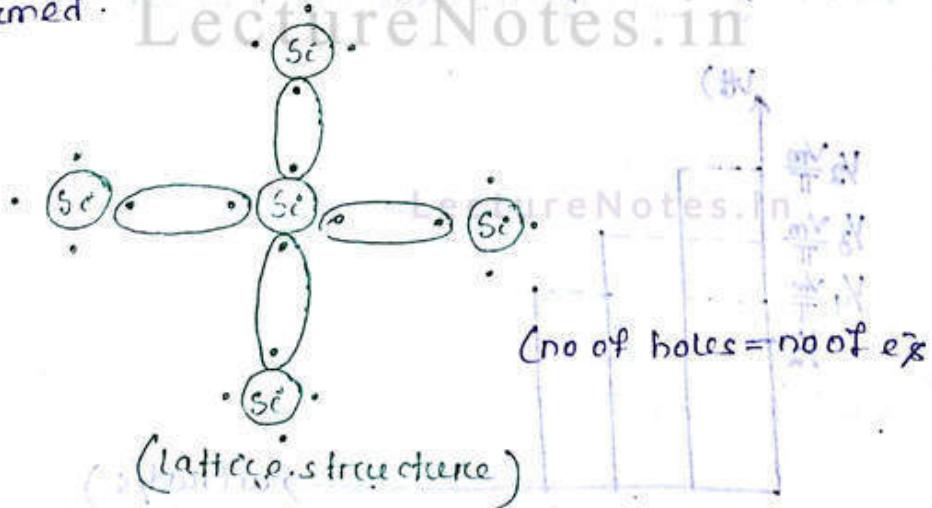x) p-type Semiconductor:



- In a p-type Semiconductor majority carriers are holes and minority carriers are e^- .
- If a trivalent impurity is added to the pure form of semiconductor, p-type Semiconductor can be formed.



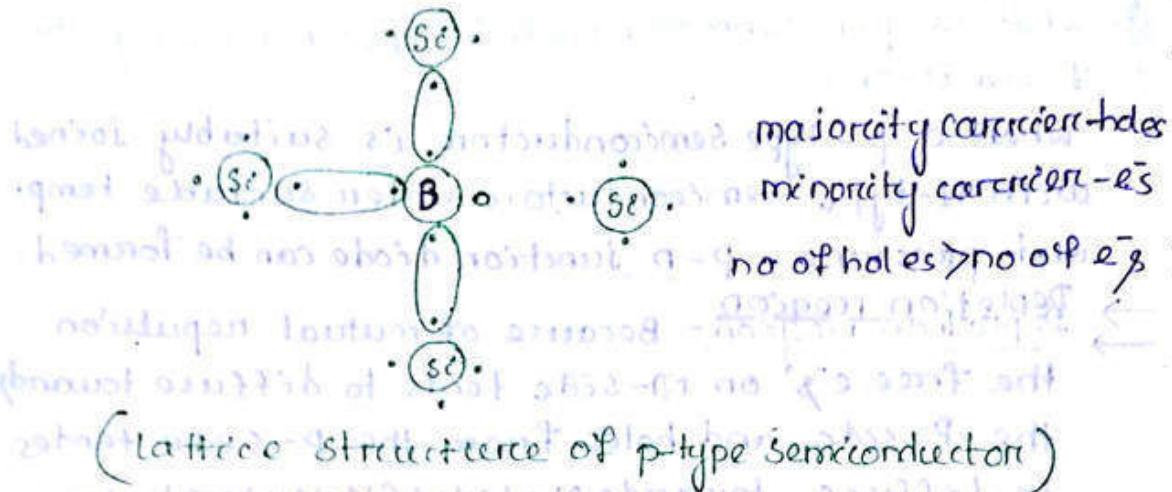

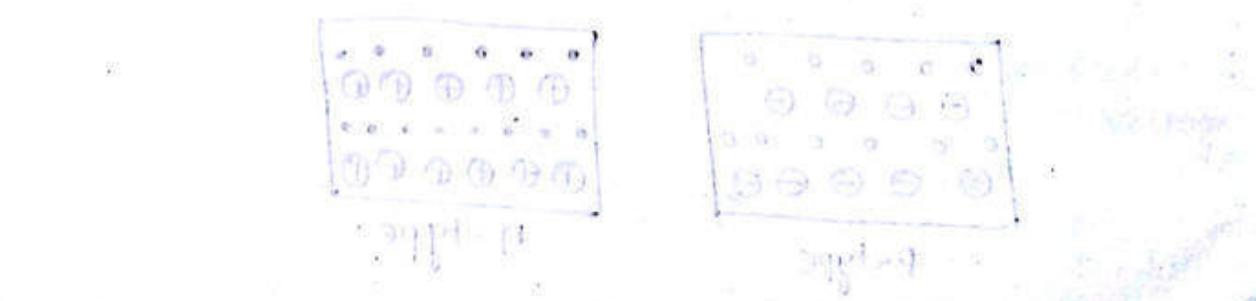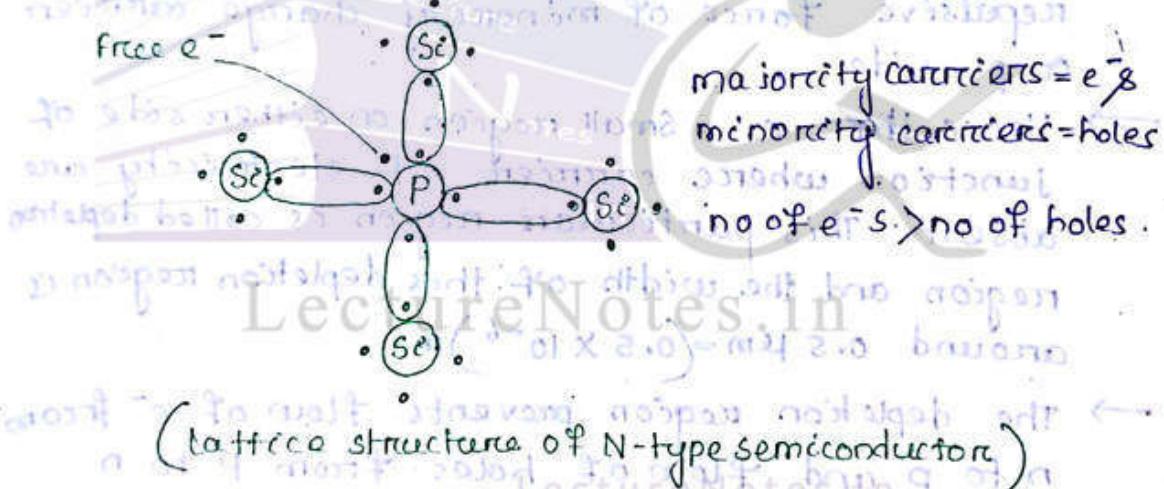
b) N-type Semiconductor:

- majority carriers are electrons
- when a pentavalent impurity such as phosphorous is added to pure form of semiconductor, N-type semiconductor can be formed.




P-N junction diode:


- Q. What is p-n junction diode? Explain briefly the formation.
- When a p-type semiconductor is suitably joined with n-type semiconductor under suitable temp. and pressure, p-n junction diode can be formed.
- Depletion region: Because of mutual repulsion the free e^- s on n-side tends to diffuse towards the p-side and holes from the p-side tends to diffuse towards n-side (Motion of holes in reality is the motion of e^- s in opposite direction).
- Ultimately a layer of -ve cons on the p-side and a layer of +ve cons on the n-side forms on the n-side forms the junction.
- Further movement of e^- s is prevented due to repulsive force of minority charge carriers on p-side.
- Hence there is a small region on either side of junction where carriers of electricity are absent. This particular region is called depletion region and the width of this depletion region is around $0.5 \mu m = (0.5 \times 10^{-6})m$.
- The depletion region prevents flow of e^- from n to p and flow of holes from p to n. Hence this region can be regarded to be providing of potential called barrier potential (V_0).
- This gives rise to electric field which prevents the movement of majority charge carriers across the junction.

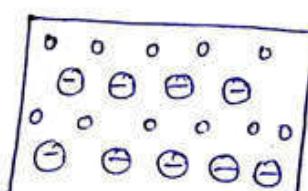

P-type

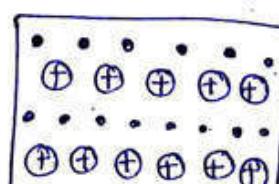

n-type

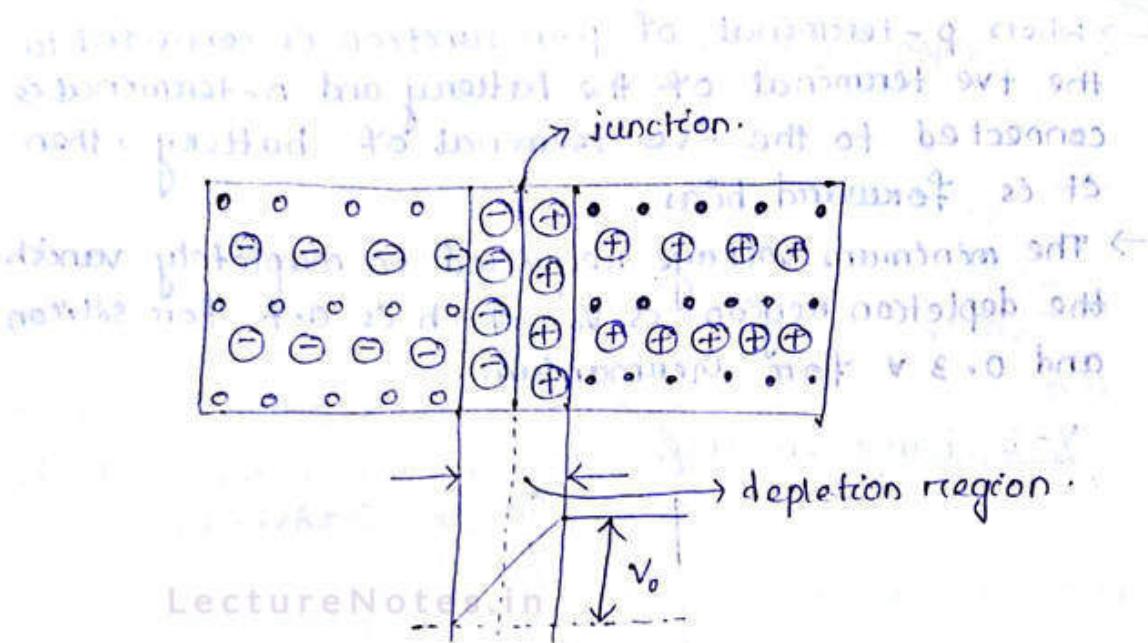

- * If p-n junction is made up of Si, then the voltage = 0.7V
- * If p-n junction is made up of Zn, then the voltage = 0.3V
- * Depletion region behaves as resistor.
- * Symbol of diode is
- * Physical representation of diode is:

Anode(A) K(cathode)


Q. What is diffusion?

→ Intermixing of two substances in particular temp. is called diffusion.

Diode under external bias:


- ↳ i) Forward bias
- ↳ ii) Reverse bias
- ↳ iii) No bias.

i) Forward bias:


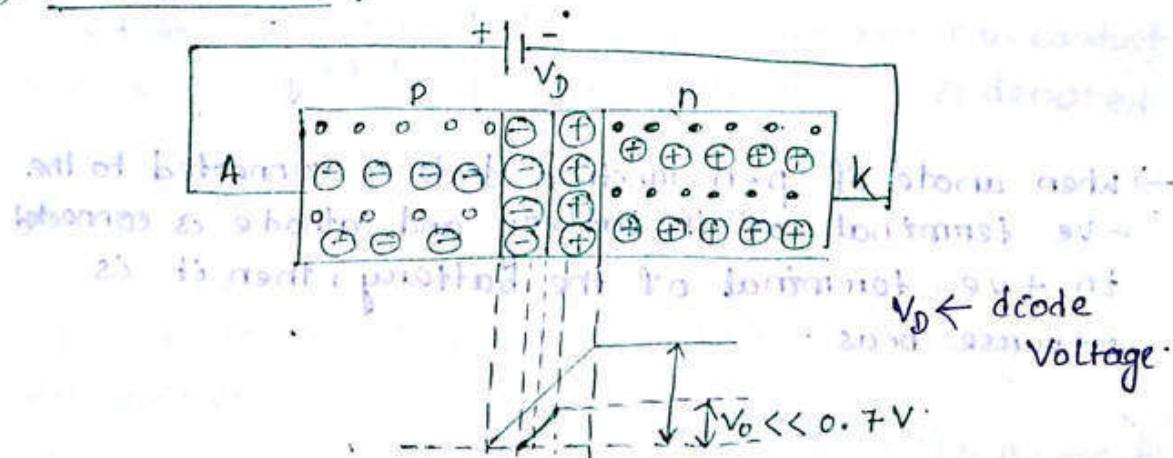


- When p-terminal of p-n junction is connected to the +ve terminal of the battery and n-terminal is connected to the -ve terminal of battery, then it is forward bias.
- The minimum voltage required to completely vanish the depletion region is V_0 which is 0.7 V for silicon and 0.3 V for germanium.

V-I characteristics

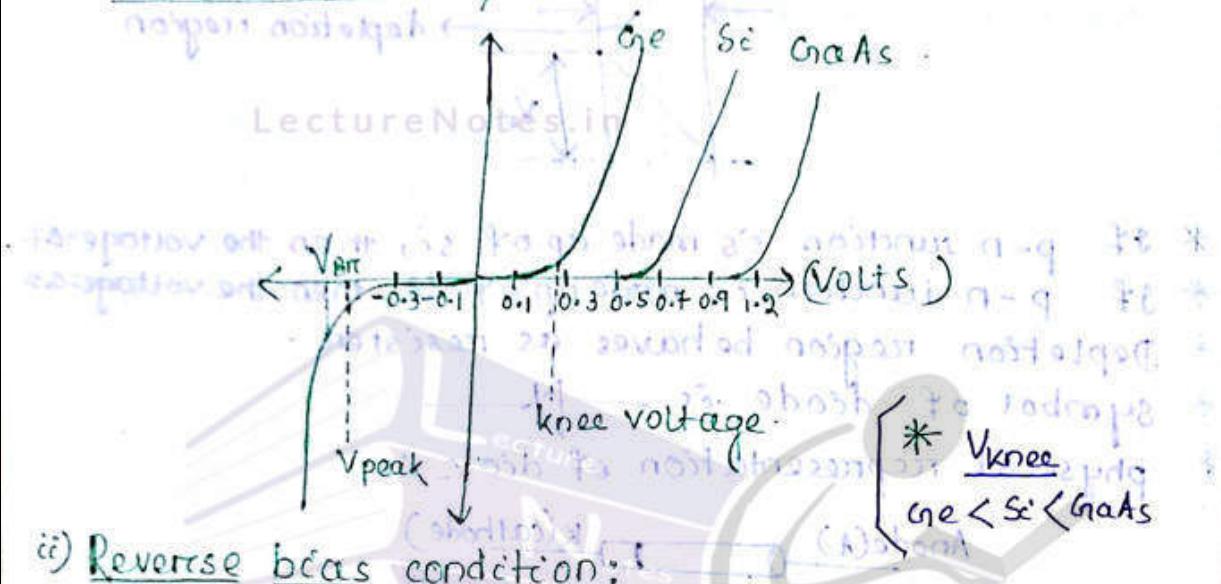

ii) Reverse bias conduction:

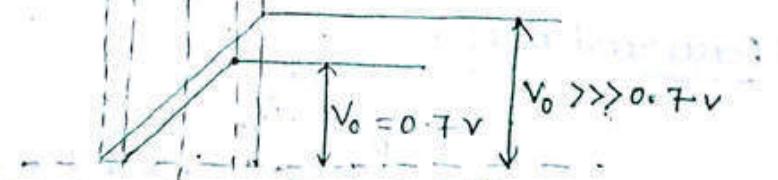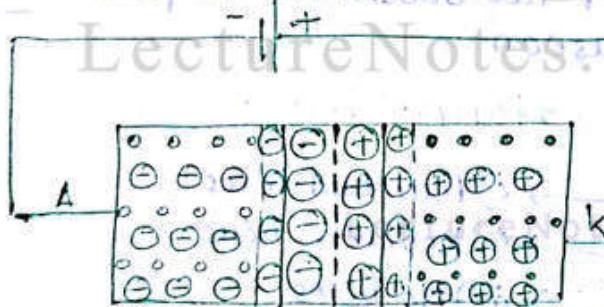

- When anode of p-n junction diode is connected to the -ve terminal of the battery and cathode is connected to +ve terminal of the battery, then it is reverse bias.

- In reverse bias condition the width of depletion layer region increases. Hence it provides very high resistance to the flow of current.
- With increase in external -ve potential the breakdown in depletion region occurs and the reverse saturation current increases at the particular breakdown voltage. The breakdown is called zener breakdown. The breakdown voltage representation is V_Z .

Q. Describe the following parameters for p-n junction diode.

- Breakdown Voltage
 - Knee voltage
 - Maximum forward current
 - Peak reverse Voltage
 - Maximum power rating
- i) Breakdown Voltage: It is the minimum reverse voltage at which the p-n junction breaks down with sudden rise in temperature and it is denoted with V_{BR} .
- ii) Knee voltage/cut-in voltage/Threshold voltage: It is the forward voltage at which current flow through junction starts to increase rapidly and denoted with V_k .
- iii) Maximum forward current: It is the highest instantaneous current in the forward direction that a p-n junction can conduct without damage to the junction, and it is denoted with I_f or I_D .
- iv) peak inverse voltage (PIV): It is the maximum reverse voltage than can be applied to the p-n junction without damage to the junction.

$$\left\{ \begin{array}{l} PIV(sic)=1000 \text{ V} \\ PIV(Ge)=400 \text{ V} \end{array} \right\} \text{in the -ve direction}$$

(v) Maximum power rating:

It is the maximum power that can be dissipated at the junction without damage to the junction. The power dissipation to the junction is equal to the product of the junction current and the voltage across the junction.

Diode Current eqⁿ:

$$I_D = I_s \left(e^{\frac{V_D}{nV_T}} - 1 \right)$$

I_D → diode current.

I_s → reverse saturation current.

V_D → external voltage.

n → ideality factor (constant). It depends upon physical construction of semiconductor.

$V_T = \frac{kT}{q}$ (Thermal voltage)

k → Boltzmann Constant = $1.38 \times 10^{-23} \text{ J/K}$

q → charge = $1.6 \times 10^{-19} \text{ C}$

T → Temp in kelvin

2. At a temperature of 27°C determine the thermal voltage in millivolt (mV).

$$\rightarrow T = 300 \text{ K}$$

$$\begin{aligned} V_T &= \frac{kT}{q} = \frac{300 \times 1.38 \times 10^{-23}}{1.6 \times 10^{-19}} \\ &= 0.02587 \text{ V} \\ &= 0.02587 \times 10^3 \text{ mV} \\ &= 25.87 \text{ mV} \end{aligned}$$

Q. The external voltage applied to the semiconductor diode is 1V and the reverse saturation is $-30 \mu A$. Find out the diode current.

$$\rightarrow V_D = 1V$$

$$I_S = -30 \times 10^{-6} A$$

$$V_T = 26 mV = 26 \times 10^{-3} V$$

$$n = 1$$

$$I_D = -30 \times 10^{-6} \left(1.6 \times 10^{-19} \left(\frac{1}{1 \times 26 \times 10^{-3}} \right) - 1 \right)$$

$$= -30 \times 10^{-6} \left(1.6 \times 10^{-19} \left(\frac{1}{26 \times 10^{-3}} \right) - 1 \right)$$

$$= 27.16 \times 10^{-3} A$$

$$= 27.16 \text{ mA}$$



$$\frac{\partial V_A}{\partial I_A} = 50 \Omega$$

Diode Resistance:

\rightarrow The p-n junction diode is a non-linear device. Hence its resistance is different at different level of applied voltage.


\rightarrow It is divided into 3 types.

i) DC/static resistance (R_D)

ii) AC/dynamic resistance (r_{ac}, r_d)

iii) Average resistance (r_{av})

c) DC Resistance:

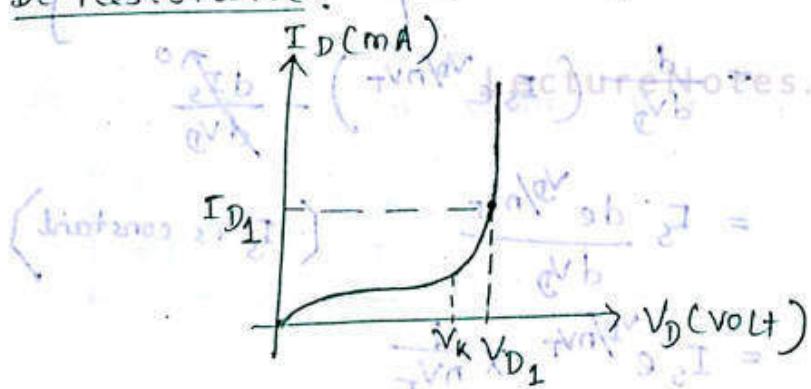


$$R_D = \frac{V_{D1}}{I_{D1}}$$

$$\frac{\partial I}{\partial V} = \frac{\partial I}{\partial V_b}$$

$$\frac{\partial V_b}{\partial I_b} = 50 \Omega$$

(c) Ac resistance:

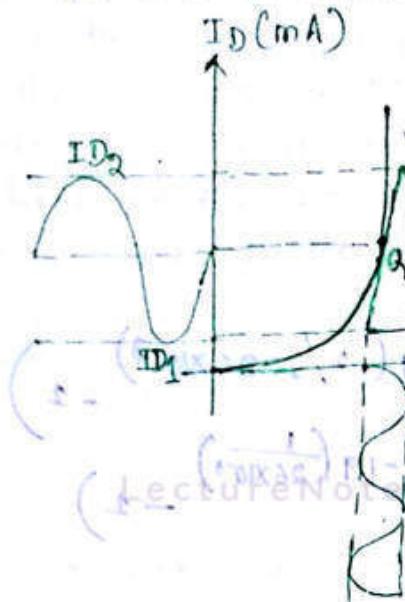

\rightarrow operating point

$$r_{ac} = \frac{\Delta V_D}{\Delta I_D}$$

\rightarrow Response of a diode to a sinusoidal input signal is defined by the tangent line at the 'Q' point.

\rightarrow

$$r_{ac} = \frac{\Delta V_D}{\Delta I_D}$$

(current eqn. of diode) $I_D = I_S (e^{V_D/nV_T} - 1)$

$$\Rightarrow \frac{dI_D}{dV_D} = \frac{d}{dV_D} \left\{ I_S e^{\frac{V_D}{nV_T}} - 1 \right\}$$

$$= \frac{d}{dV_D} \left(I_S e^{\frac{V_D}{nV_T}} \right) - \frac{d}{dV_D} 1$$

$$= I_S \frac{d e^{\frac{V_D}{nV_T}}}{dV_D} \quad (I_S \text{ is constant})$$

$$= I_S e^{\frac{V_D}{nV_T}} \times \frac{1}{nV_T}$$

$$\frac{dI_D}{dV_D} = \frac{I_S}{nV_T} \times e^{\frac{V_D}{nV_T}}$$

$$r_{ac} = \frac{dV_D}{dI_D}$$

$$\frac{dI_D}{dV_D} = I_s \left(\frac{1}{nV_T} e^{\frac{V_D}{nV_T}} \right)$$

$$= I_s \left(\frac{e^{\frac{V_D}{nV_T}}}{nV_T} \right)$$

$$\frac{dI_D}{dV_D} = \frac{I_s (e^{\frac{V_D}{nV_T}} - 1 + 1)}{nV_T}$$

$$= \frac{I_s (e^{\frac{V_D}{nV_T}} - 1)}{nV_T} + I_s$$

Lecture Notes

$$\frac{dI_D}{dV_D} = \frac{I_D + I_S}{nV_T}$$

$$\Rightarrow \frac{dV_D}{dI_D} = \frac{nV_T}{I_D + I_S}$$

we know, $n = 1$


$$\text{Hence } \frac{dV_D}{dI_D} = \frac{V_T}{I_D + I_S}$$

At room temperature (25°C) $V_T \approx 26\text{ mV}$.

$$\text{so, } \frac{dV_D}{dI_D} = \frac{26\text{ mV}}{I_D + I_S}$$

Since $I_D \gg I_S$, the value of I_S can be neglected
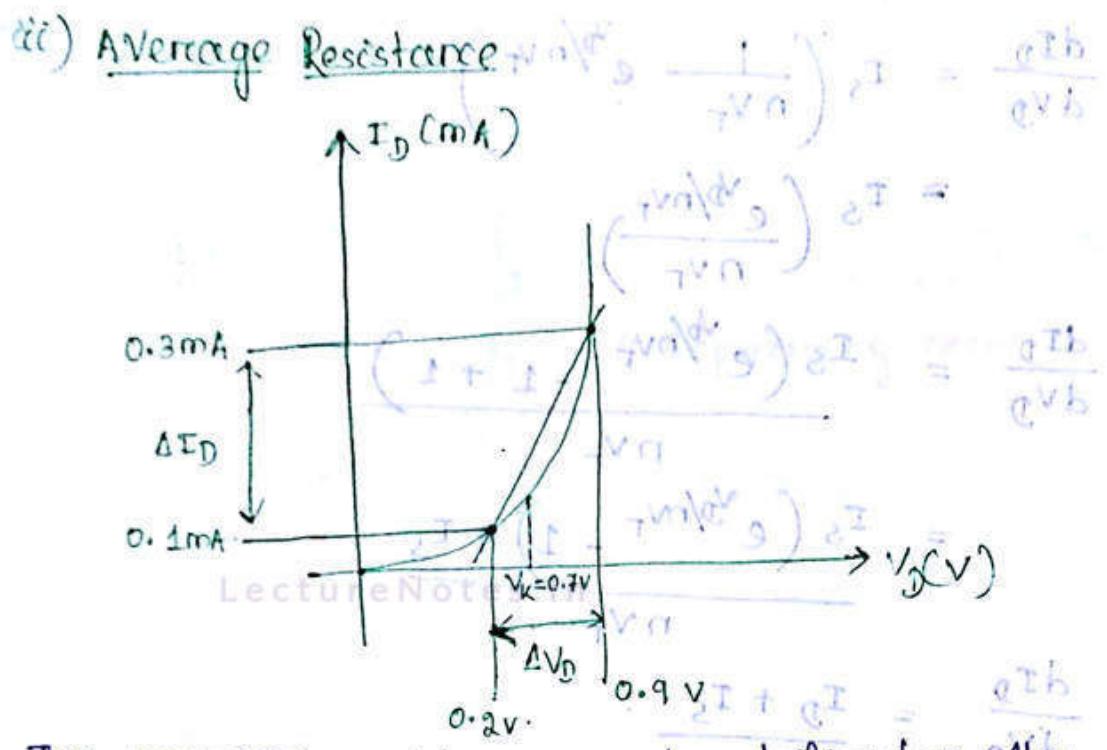
$$\boxed{\frac{dV_D}{dI_D} = \frac{26\text{ mV}}{I_D}}$$



The average resistance can be defined as the resistance calculated by a straightline drawn between two intersection point established by maximum and minimum value of c/p.

$$R_{av} = \frac{\Delta V_D}{\Delta I_D} \quad \begin{matrix} \text{Notes} \\ \text{point to point} \end{matrix}$$

$$R_{av} = \frac{(0.9 - 0.2)V}{(0.3 - 0.1)mA \times 10^{-3}}$$

$$= \frac{0.7}{0.2 \times 10^{-3}} \quad \begin{matrix} \text{Notes} \\ \text{small current} \end{matrix}$$


$$= 3500 \Omega$$

Diode equivalent Circuit:

- An equivalent circuit is a combination of electronic components or elements properly chosen to represent the actual characteristics of a system or device in a particular operating region.
- Diode equivalent circuits are divided into 3 types.

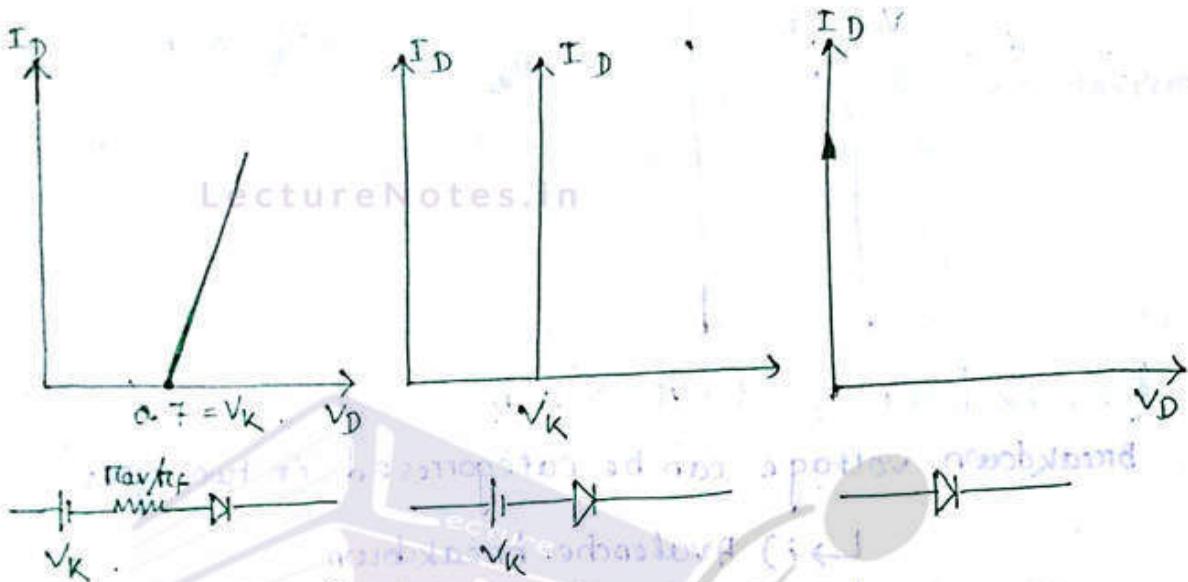
- (i) piece wise linear equivalent ckt
- (ii) simplified equivalent ckt
- (iii) Ideal equivalent ckt


Piecewise Linear equivalent Model Simplified equivalent model Ideal equivalent model



Effect of temperature on diode current

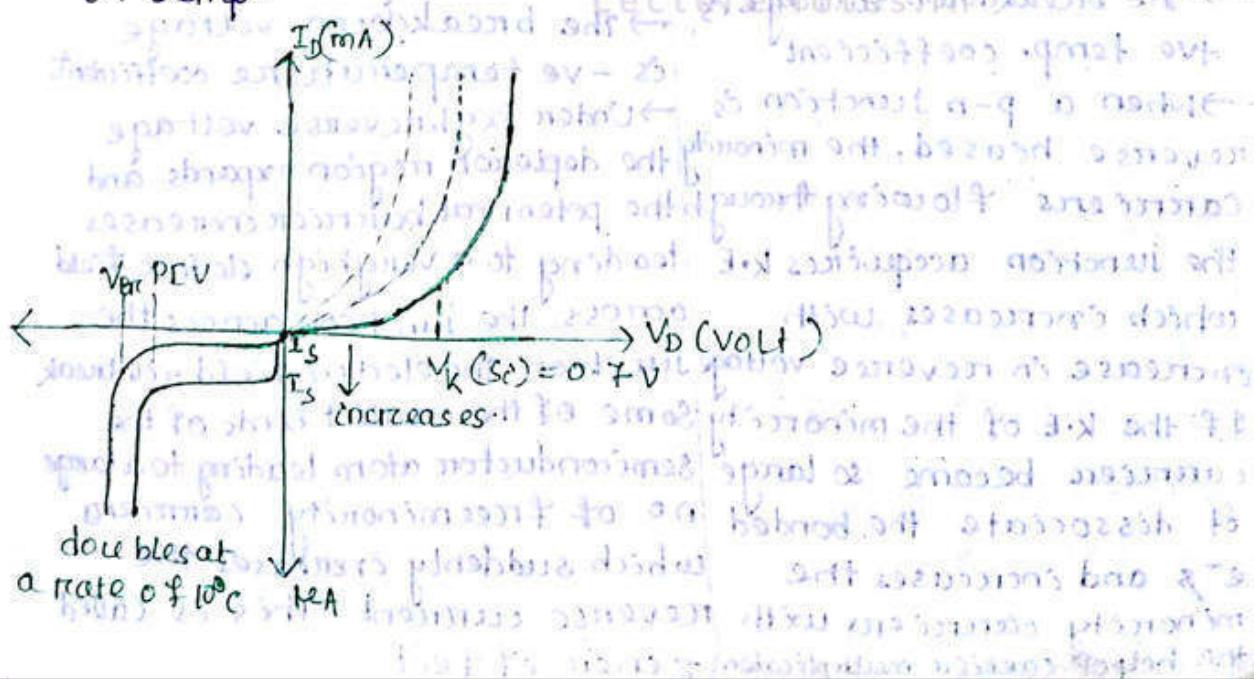- In the forward bias region the characteristics of a si diode shifts to the left at a rate of 2.5 mV per degree rise in temp.
- In the reverse bias region the reverse saturation current of si diode doubles for every 10°C rise in temp.



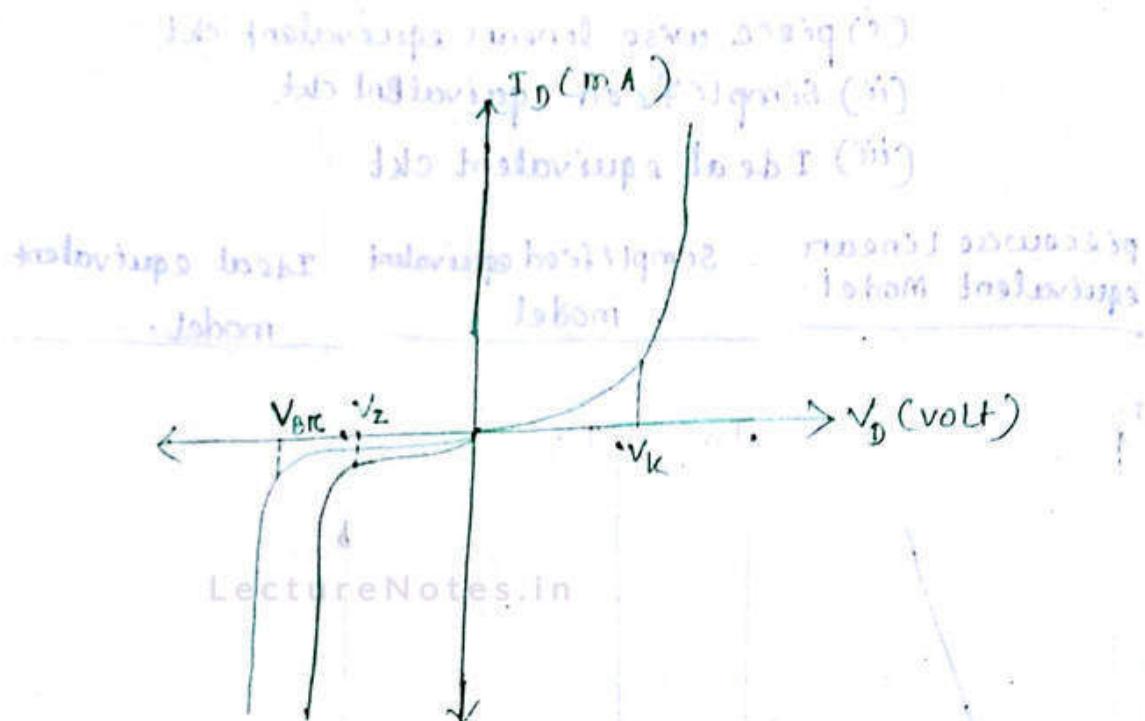

Breakdown voltage:

Breakdown voltage can be categorised in two types.

↳ i) Avalanche breakdown.

↳ ii) Zener breakdown.

Avalanche breakdown

- It is lightly doped.
- Avalanche breakdown has high reverse voltage.
- Breakdown occurs due to carrier multiplication.
- The breakdown voltage has +ve temp. coefficient.
- When a p-n junction is reverse biased, the minority carriers flowing through the junction acquires k.E which increases with increase in reverse voltage. If the k.E of the minority carriers become so large it dissociate the bonded e⁻ & p and increases the minority carriers with the help of carrier multiplication.

Zener breakdown

- It is heavily doped.
- It has low reverse breakdown voltage.
- Breakdown occurs due to high electric field.
- The breakdown voltage has -ve temperature coefficient.
- Under high reverse voltage the depletion region expands and the potential barrier increases leading to a very high electric field across the junction. The electric field will break some of the covalent bonds of the semiconductor atom leading to a large no. of free minority carriers which suddenly increases the reverse current. This is called zener effect.


5:

CHE

- $V_K = 0.7 \text{ V}$ $\rightarrow V_K = 0.3 \text{ V}$
- high temperature sensitive \rightarrow less temperature sensitive
- $P_{EV} (\text{silicon}) \rightarrow 1000 \text{ V}$ $\rightarrow P_{EV} (\text{CIE}) \rightarrow 400 \text{ V}$
- reverse saturation current $\rightarrow 10^{-9} \text{ A}$ \rightarrow reverse saturation current $\rightarrow 10^{-6} \text{ A}$
- Ex: sc type semiconductor \rightarrow Ex: opto electronic devices, rectifier, clippers, clampers

Amplifier in cascade:

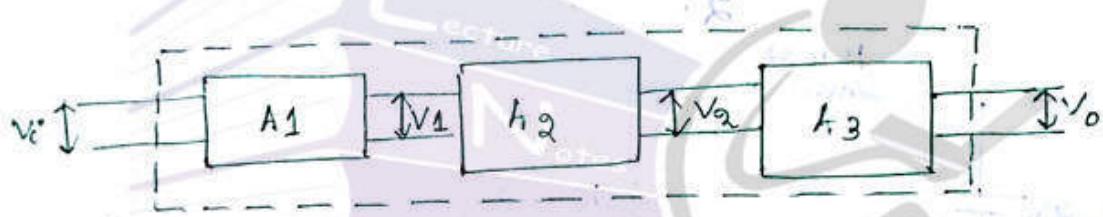If more than one amplifiers are connected in series, then that particular arrangement is called amplifiers in cascade.



$$AV_{(\text{total})} = \frac{V_o}{V_i}$$

$$AV_1 = \frac{V_1}{V_i}$$

$$AV_2 = \frac{V_2}{V_1}$$

$$AV_3 = \frac{V_o}{V_2}$$

$$AV_1 \times AV_2 \times AV_3$$

$$= \frac{Y_1}{V_i} \times \frac{Y_2}{Y_1} \times \frac{Y_o}{Y_2} = \frac{V_o}{V_i} = AV_{(\text{total})}$$

$$AV_{(\text{total})} = AV_1 \times AV_2 \times AV_3 \times \dots \times AV_n$$

$$\Rightarrow 20 \log AV_{(\text{total})} = 20 \log (AV_1 \times AV_2 \times \dots \times AV_n)$$

$$\Rightarrow 20 \log AV_{(\text{total})} = 20 \log AV_1 + 20 \log AV_2 + \dots + 20 \log AV_n$$

$$\Rightarrow [AV_{(\text{total})}(\text{dB}) = AV_1(\text{dB}) + AV_2(\text{dB}) + \dots + AV_n(\text{dB})]$$

$$* P = V \cdot I$$

$$P_o = V_o I_o$$

$$P_i = V_i I_i$$

$$A_p (\text{dB}) = 10 \log \left(\frac{P_o}{P_i} \right)$$

$$= 10 \log \left(\frac{V_o I_o}{V_i I_i} \right)$$


$$= 10 \log \left\{ \left(\frac{V_o}{V_i} \right) \times \left(\frac{I_o}{I_i} \right) \right\}$$

$$= 10 \log \left(\frac{V_o}{V_i} \right) + 10 \log \left(\frac{I_o}{I_i} \right)$$

$$A_p (\text{dB}) = 20 \log \left(\frac{V_o}{V_i} \right) + 20 \log \left(\frac{I_o}{I_i} \right)$$

$$A_p (\text{dB}) = A_v (\text{dB}) + A_c (\text{dB})$$

Q.

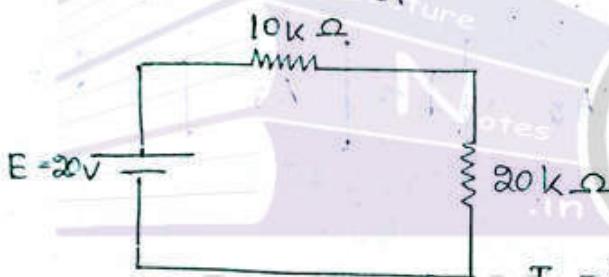

$$R = R_1 + R_2$$

$$= 10 \times 10^3 + 20 \times 10^3$$

$$= 30$$

$$I = \frac{E}{R} = \frac{20}{30 \times 10^3} = 0.6 \times 10^{-3} \text{ A.}$$

OR

According to KVL


$$E - IR_1 - IR_2 = 0 \quad (\because \text{In series connection current flow remains same})$$

$$\Rightarrow E = I (R_1 + R_2)$$

$$\Rightarrow I = \frac{E}{R_1 + R_2}$$

$$\Rightarrow I = \frac{20}{30 \times 10^3} = 0.6 \times 10^{-3} \text{ A.}$$

A.

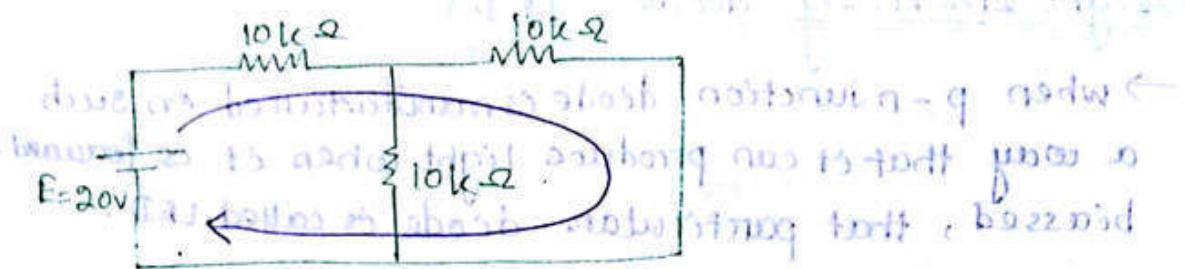

→ According to KVL,

$$E - IR_1 - IR_2 = 0$$

$$\Rightarrow E = I(R_1 + R_2)$$

$$\Rightarrow E = I(10 + 10)$$

$$\Rightarrow E = 20 \text{ V}$$


$$\Rightarrow \frac{E}{I} = 20 \Omega$$

$$\Rightarrow \frac{R_1 + R_2}{I} = 20 \Omega$$

$$\Rightarrow R = 20 \Omega$$

$$I = \frac{E}{R} = \frac{20}{20 \times 10^3} = 10^{-3} \text{ A}$$

B.

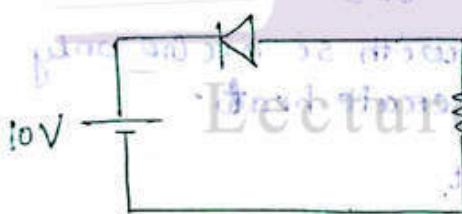

→ It is in reverse bias condition

$$I_R = 0, I_D = 0$$


$$V_R = I_D \times R = 0$$

$$V_D = 10 \text{ V} = \text{initial value}$$



Light Emitting diode (LED)

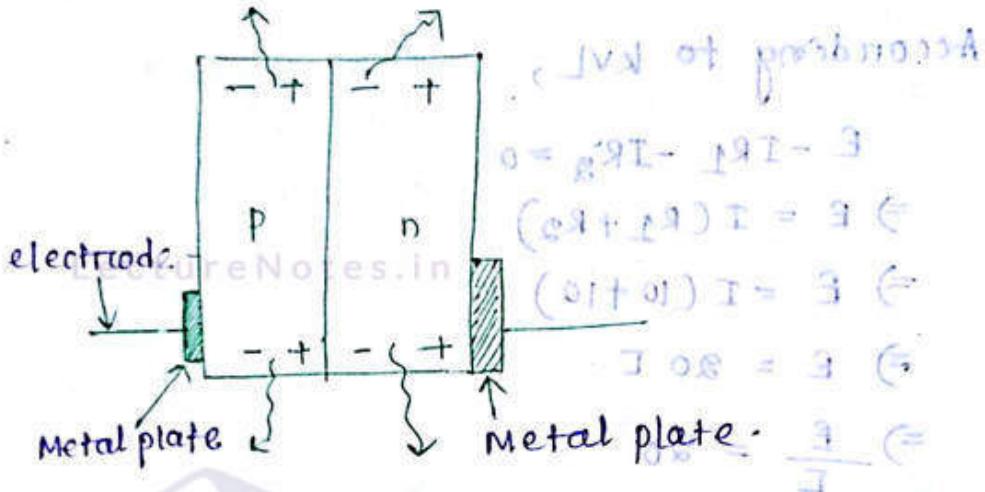→ When p-n junction diode is manufactured in such a way that it can produce light when it is forward biased, that particular diode is called LED.



→ When a diode is forward biased the electrons from n-side combines with holes of the p-side. With this combination there is a generation of heat. Ultimately it generates light when it is over heated. Due to the property of emitted light, these type of diodes are called LED.

→ A diode manufactured with Si or Ge only has the capability to generate heat.


→ It can not produce light.


→ Some compound semiconductors such as GaAs, GaN, GaP, GaAsP has the capability to generate light in forward biasing mode.

→ GaAs emits Red colour. GaP emits Green colour. GaN emits white colour. GaAsP emits orange.

Zener diode :

Symbol:

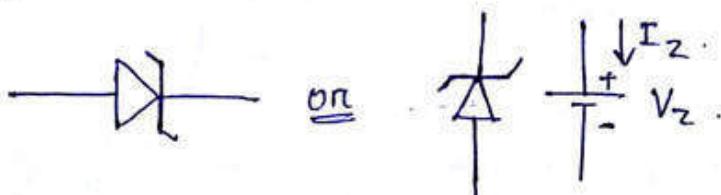

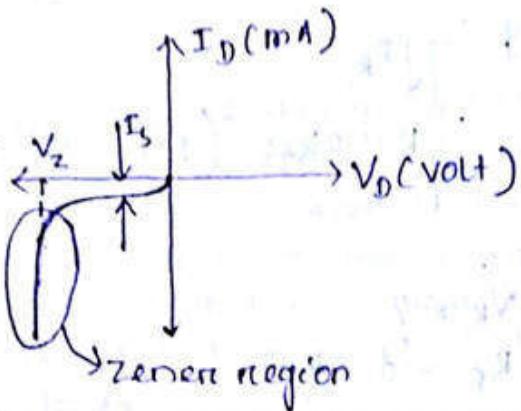


- When a diode is reverse biased after particular voltage, the reverse saturation current increases suddenly in the reverse direction.
- If doping level of a semiconductor can be increased, the breakdown voltage can be acquired very soon. This particular breakdown voltage is called zener voltage and the device which operated in this zener voltage is called zener diode.
- While increasing doping level of the semiconductor we assure that diode is not going to burn out or destroy.
- Application of zener diode is voltage regulator.
- Zener diode has two states.

i) ON state


& OFF state.


c) ON state:

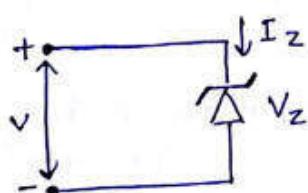

If $V > V_Z$, diode is ON and it is conducting current.

d) OFF state: (If $V < V_Z$)

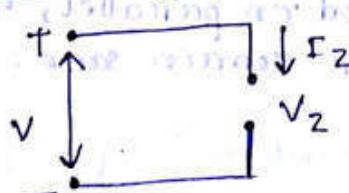

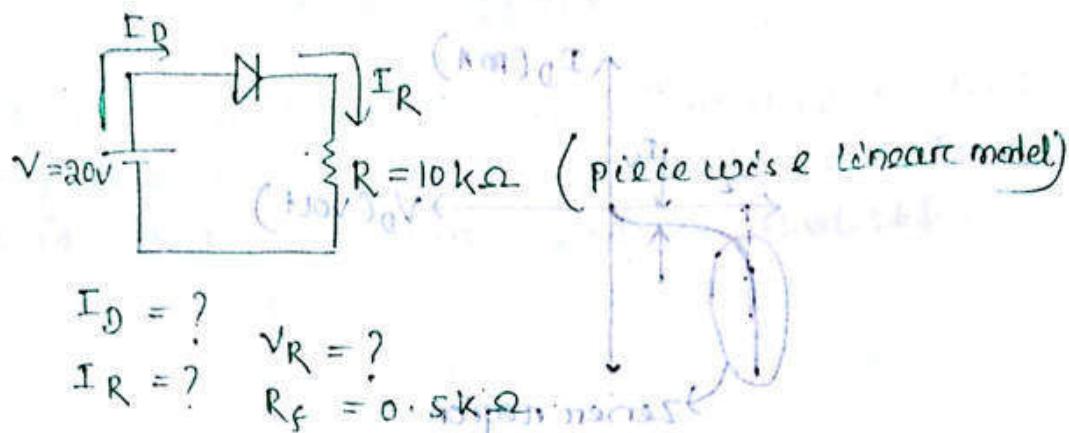

$$I_D = ? \quad V_R = ?$$

$$I_R = ?$$

$$R_f = 0.5k\Omega$$

→ multiplying $0.7V_0$ here $R_f = 0.5k\Omega$ can be short as nothing
is changing in the circuit so we can ignore it, option
with permission of finishing a second time
because it's not important and no option available and
option notes after option available and continuing first
option. $I_D = I_R$ (\because when resistors are in series, the total
current in each resistor remains same)


According to Kirchoff's law, the total current entering the node is equal to the total current leaving the node.

$$\begin{aligned} 20 - 0.7 - (I_D \times 0.5) - (I_D \times 10) &= 0 \\ \Rightarrow 19.3 - (10.5 I_D) &= 0 \\ \Rightarrow 10.5 I_D &= 19.3 \\ \Rightarrow I_D &= \frac{19.3}{10.5} = 1.838 \text{ mA} \end{aligned}$$

$$I_R = 1.838$$

$$\begin{aligned} V_R &= I_D \times R \\ &= 1.838 \times 10k\Omega \\ &= 18.38 \text{ V} \end{aligned}$$

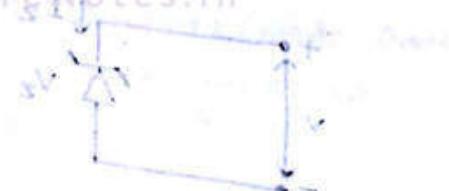- * When resistors are in series, the current across the resistors remains same.
- * When resistors are connected in parallel, the voltage across the resistors remain same.



Rectifiers:

→ \hookrightarrow Half wave Rectifier (HWR)

\hookrightarrow Full wave Rectifier (FWR)


Full wave rectifier (FWR) :

\hookrightarrow Centre tap full wave rectifier

\hookrightarrow Full wave bridge type rectifier

→ Rectifiers are electronic ckt which converts


i/p ac signal into pulsating dc

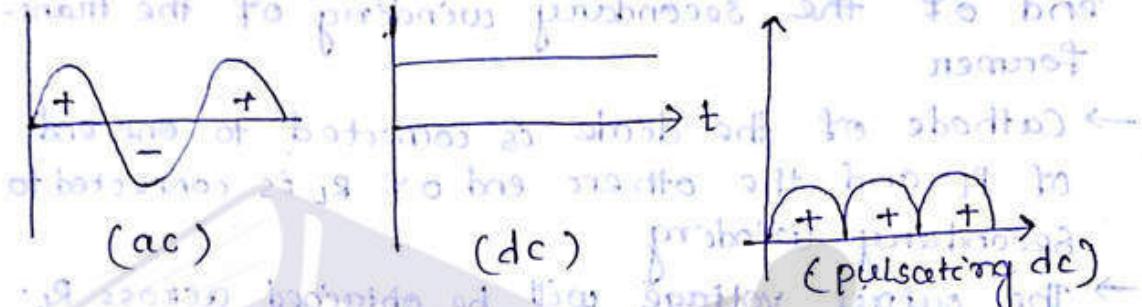

→ Fan, heater, bulbs, air conditioner, etc run with the help of ac signal. But there are some devices which can not be run with the help of ac signal such as mobile phones, toy cars, walk-man, mini emergency light, torch light etc. These equipments can be run with the help of dc supply.

→ As ac signal is generally available to run these equipments (electronic equipments), ac is converted to dc.

Half-wave rectifier (HWR) :

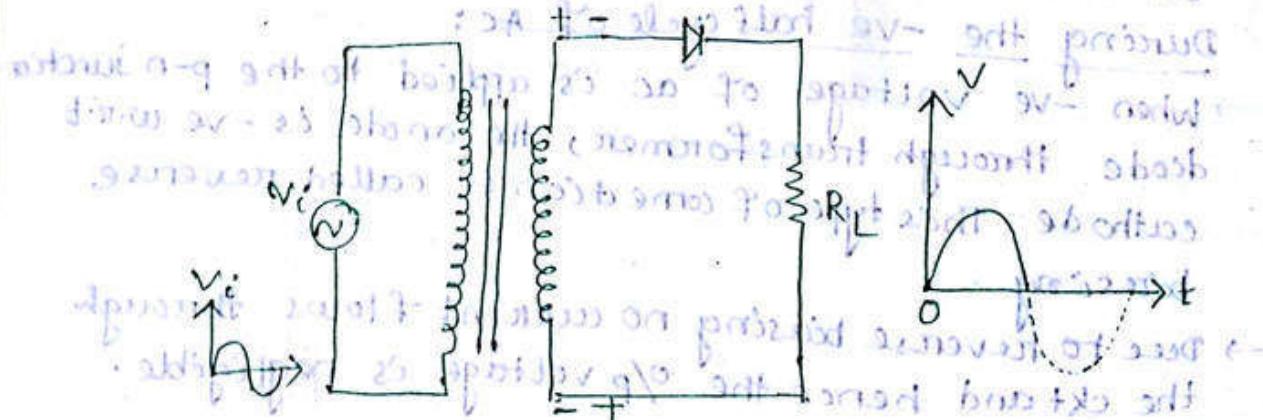

Statement:

The type of rectifiers in which the o/p current flow corresponding to one half cycle of the i/p alternating current is called HWR.

Construction:

- It consists of a single p-n junction diode
- The ac supply is to be rectified through a transformer in series with diode and load register (R_L)
- The anode of the diode is connected to one end of the secondary winding of the transformer
- Cathode of the diode is connected to one end of R_L and the other end of R_L is connected to Secondary winding.
- The output voltage will be obtained across R_L .

Working:

During +ve half cycle of Ac:


- When +ve half of i/p ac is applied through transformer, then anode of the p-n junction diode becomes +ve w.r.t. cathode. This type of connection is called forward biasing.
- Due to forward biasing current flows through the circuit.
- When the resulting current flows through the load resistor (R_L), the o/p voltage is obtained.

During the -ve half cycle of Ac:

- When -ve voltage of ac is applied to the p-n junction diode through transformer, the anode is -ve w.r.t. cathode. This type of connection is called reverse biasing.
- Due to reverse biasing no current flows through the ckt and hence the o/p voltage is negligible.

Conclusion:

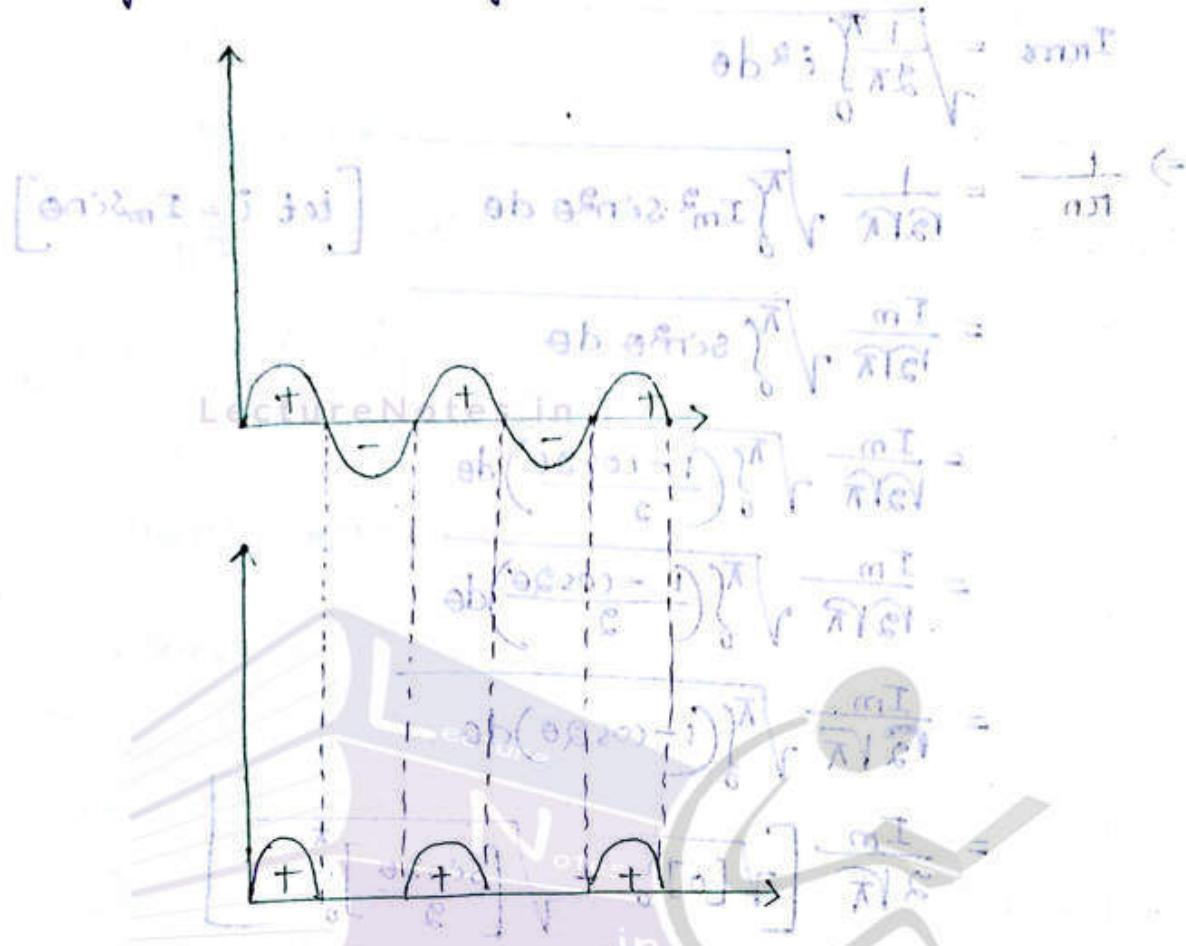In HWR, current flows through R_L during the two half cycles of ac only. Hence it is unidirectional.



Disadvantage of HWR:

In HWR the flow of o/p power is due to the half cycle of the c/p signal only. Other halfcycle is wasted.

Calculation of I_{dc} in HWR: $\frac{I_m}{\pi} \times \frac{\pi}{2} = 2I_{dc}$

$$\begin{aligned}
 I_{dc} &= \frac{1}{2\pi} \int_0^\pi i_m d\theta \\
 &= \frac{1}{2\pi} \int_0^\pi I_m \sin \theta d\theta \\
 &\quad \left[\text{Let } i = I_m \sin \theta \right] \\
 &= \frac{I_m}{2\pi} \int_0^\pi \sin \theta d\theta \\
 &\quad \left[\text{For } \int \sin \theta d\theta = [-\cos \theta] \right] \\
 &= \frac{I_m}{2\pi} \cdot [-\cos \theta]_0^\pi \\
 &= \frac{I_m}{2\pi} \left[-\cos \pi - (-\cos 0) \right] = \frac{I_m}{2\pi} \times 2 = \frac{I_m}{\pi}
 \end{aligned}$$

$$I_{dc} = \frac{I_m}{\pi}$$

~~more about it depends upon the following result of~~
calculation of I_{rms} in HWR: ~~to be done~~

$$I_{rms} = \sqrt{\frac{1}{2\pi} \int_0^\pi i^2 d\theta}$$

$$\Rightarrow I_{rms} = \frac{1}{\sqrt{2\pi}} \sqrt{\pi \int_0^\pi I_m^2 \sin^2 \theta d\theta} \quad [\text{let } i = I_m \sin \theta]$$

$$= \frac{I_m}{\sqrt{2\pi}} \sqrt{\pi \int_0^\pi \sin^2 \theta d\theta}$$

LectureNotes.in

$$= \frac{I_m}{\sqrt{2\pi}} \sqrt{\pi \int_0^\pi \left(\frac{1-\cos 2\theta}{2}\right) d\theta}$$

$$= \frac{I_m}{\sqrt{2\pi}} \sqrt{\pi \int_0^\pi \left(\frac{1-\cos 2\theta}{2}\right) d\theta}$$

$$= \frac{I_m}{\sqrt{2\pi}} \sqrt{\pi \int_0^\pi (1-\cos 2\theta) d\theta}$$

$$= \frac{I_m}{\sqrt{2\pi}} \left[\sqrt{\int_0^\pi (1-\cos 2\theta) d\theta} \right]$$

$$= \frac{I_m}{\sqrt{2\pi}} \left[\sqrt{(0-\pi)} - \sqrt{\left[\frac{\sin 2\theta}{2}\right]_0^\pi} \right]$$

$$I_{rms} = \frac{I_m}{\sqrt{2\pi}} \times \sqrt{\pi} = \frac{I_m}{2}$$

calculation of efficiency in HWR:

efficiency (η) = $\frac{\text{dc o/p power}}{\text{ac o/p power}}$

$$= \frac{I_{dc}^2 \times R_L}{I_{rms}^2 (R_L + r_f)}$$

$$= \frac{I_{dc}^2 \times R_L}{I_{rms}^2 \times R_L} \quad [\because R_L \ggg r_f]$$

$$\begin{aligned}
 & \frac{I_{dc}^2}{I_{rms}^2} = \frac{\left(\frac{I_m}{\pi}\right)^2}{\left(\frac{I_m}{2}\right)^2} \\
 & = \frac{I_m^2 \times 4}{I_m^2 \times \pi^2} \\
 & = \frac{4}{\pi^2} = 40.5\%
 \end{aligned}$$

$$n_{HWR} = 40.5\%$$

Ripple factor in HWR:

Ripple factor in HWR = $\frac{I_{ac}}{I_{dc}}$

$$I_{rms}^2 = I_{dc}^2 + I_{ac}^2$$

$$\text{or } I_{ac} = \sqrt{I_{rms}^2 - I_{dc}^2}$$

Dividing both sides by I_{dc}

$$\frac{I_{ac}}{I_{dc}} = \sqrt{\left(\frac{I_{rms}}{I_{dc}}\right)^2 - 1}$$

$$\frac{I_{ac}}{I_{dc}} = \sqrt{\frac{\left(\frac{I_m}{2}\right)^2}{\left(\frac{I_m}{\pi}\right)^2} - 1}$$


$$\frac{I_{ac}}{I_{dc}} = \sqrt{\frac{\pi^2}{4} - 1}$$

$$\frac{I_{ac}}{I_{dc}} = 1.21$$

$$I_{dc}$$

$$\text{Ripple factor of HWR} = 1.21$$

Centre tap FWR :

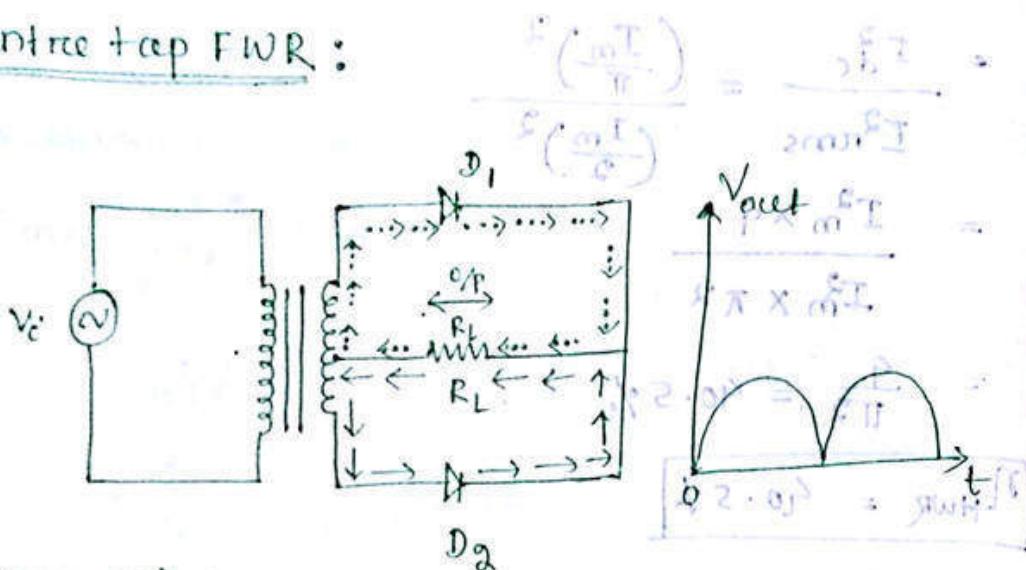

Statement :

→ A rectifier in which current flows through the load resistor (\$R_L\$) for both the halves of c/p ac signal is called FWR.

construction :

- It consists of two p-n junction diodes.
- The anodes of two diodes are connected to the opposite ends of centre tapped secondary winding.
- The two cathodes of two diodes are connected to one side of load resistor (\$R_L\$).
- The other end of \$R_L\$ is connected to the centre-tapped secondary winding.
- Only one half of transformer's secondary voltages appear between the anode and cathode of each diode.
- The o/p voltage will be obtained across \$R_L\$.

Working :

During +ve half cycle of ac signal:

- When +ve half cycle of ac signal is applied, the upper half of secondary becomes +ve w.r.t lower half.
- Now the diode \$D_1\$ is forward biased and hence current flows through the load resistor \$R_L\$. Hence o/p voltage will be obtained across \$R_L\$.

- At the same time the anode of the diode D_2 is -ve w.r.t cathode which is called reverse biasing.
- Due to reverse biasing, no current results hence no o/p voltage will be obtained across R_L .

During -ve halfcycle of ac signal:

- During the -ve halfcycle of secondary voltage, the upper half of the secondary winding becomes -ve w.r.t lower half. Now the diode D_1 becomes reverse biased i.e. anode is -ve w.r.t cathode.

Therefore current does not take place in diode D_1 . Hence o/p voltage across R_L is zero.

- But at the same time, the diode D_2 is forward biased i.e. anode is +ve w.r.t cathode. Due to forward biasing, current flows through the load R_L and hence the voltage will be obtained across it.

Conclusion:

Current flows for both halfcycles of ac signal through the ckt. and hence we get DC O/P:

Calculation of I_{dc} in centretapped FWR:

$$I_{dc} = \frac{1}{\pi} \int_0^{\pi} i d\theta$$

$$\Rightarrow I_{dc} = \frac{1}{\pi} \int_0^{\pi} I_m \sin \theta d\theta \quad [i = I_m \sin \theta]$$

$$\Rightarrow I_{dc} = \frac{I_m}{\pi} \int_0^{\pi} \sin \theta d\theta$$

$$\Rightarrow I_{dc} = \frac{I_m}{\pi} [-\cos \theta]_0^{\pi}$$

$$\Rightarrow I_{dc} = \frac{I_m}{\pi} [-\cos \pi - (-\cos 0)]$$

$$\Rightarrow I_{dc} = \frac{I_m}{\pi} (2)$$

$$\Rightarrow \boxed{I_{dc} = \frac{2I_m}{\pi}}$$

Calculation of I_{rms} in centretapped FWR

$$I_{rms} = \sqrt{\frac{1}{\pi} \int_0^{\pi} I_m^2 \sin^2 \theta} \quad \text{[positive amount of angle]}$$

$$I_{rms} = \frac{1}{\pi} \sqrt{\int_0^{\pi} I_m^2 \sin^2 \theta} \quad \text{[Let } I_m = \text{const.]} \quad \text{[positive portion of the alternating current is present]}$$

$$I_{rms} = \frac{I_m}{\pi} \sqrt{\int_0^{\pi} \sin^2 \theta} \quad \text{[positive portion of the alternating current is present]}$$

$$I_{rms} = \frac{I_m}{\pi} \sqrt{\int_0^{\pi} \frac{1 - \cos 2\theta}{2}} \quad \text{[positive portion of the alternating current is present]}$$

$$I_{rms} = \frac{I_m}{\pi} \sqrt{\frac{1}{2} \int_0^{\pi} d\theta - \int_0^{\pi} \cos 2\theta d\theta} \quad \text{[positive portion of the alternating current is present]}$$

$$I_{rms} = \frac{I_m}{\pi \sqrt{2}} \sqrt{\int_0^{\pi} d\theta - \int_0^{\pi} \cos 2\theta d\theta} \quad \text{[positive portion of the alternating current is present]}$$

$$I_{rms} = \frac{I_m}{\pi \sqrt{2}} \left[\sqrt{\int_0^{\pi} d\theta} - \sqrt{\int_0^{\pi} \cos 2\theta d\theta} \right] \quad \text{[positive portion of the alternating current is present]}$$

$$I_{rms} = \frac{I_m}{\pi \sqrt{2}} \left[\sqrt{[\theta]_0^\pi} - \sqrt{\left[\frac{\sin 2\theta}{2} \right]_0^\pi} \right] \quad \text{[positive portion of the alternating current is present]}$$

$$I_{rms} = \frac{I_m}{\pi \sqrt{2}} \left[\sqrt{\pi - 0} - \sqrt{\frac{\sin 2\pi}{2} - 0} \right] \quad \text{[positive portion of the alternating current is present]}$$

$$I_{rms} = \frac{I_m}{\pi \sqrt{2}} \times \sqrt{\pi} \quad \text{[positive portion of the alternating current is present]}$$

$$I_{rms} = \frac{I_m}{\sqrt{2}} \quad \text{[positive portion of the alternating current is present]}$$

Calculation of efficiency in FWR:

$$\text{efficiency}(\eta) = \frac{\text{DC power output}}{\text{I/P ac power}}$$

$$= \frac{I_{dc}^2 R_L}{I_{rms}^2 (R_L + r_f)}$$

$$= \frac{\frac{4 I_m^2}{\pi^2}}{\frac{I_m^2}{2}}$$

$$= \frac{4I_m^2}{\pi^2} \times \frac{3}{I_m^2}$$

$$= \frac{8}{\pi^2}$$

∴ ripple factor = $\sqrt{\frac{8}{\pi^2}} = 0.48$

$$= \frac{2A}{7} \times \frac{2A}{7} = 0.48$$

$$= 0.81 \text{ A.}$$

$$= 81 \text{ V.}$$


Calculation of Ripple Factor on centre tapped FWR:

$$\frac{I_{ac}}{I_{dc}} = \sqrt{\left(\frac{I_{rms}}{I_{dc}}\right)^2 - 1}$$

$$= \sqrt{\frac{\left(\frac{I_m}{\sqrt{2}}\right)^2}{\left(\frac{2I_m}{\pi}\right)^2} - 1} = 0.48$$

Ripple factor of centretapped FWR = 0.48

Bridge type FWR:

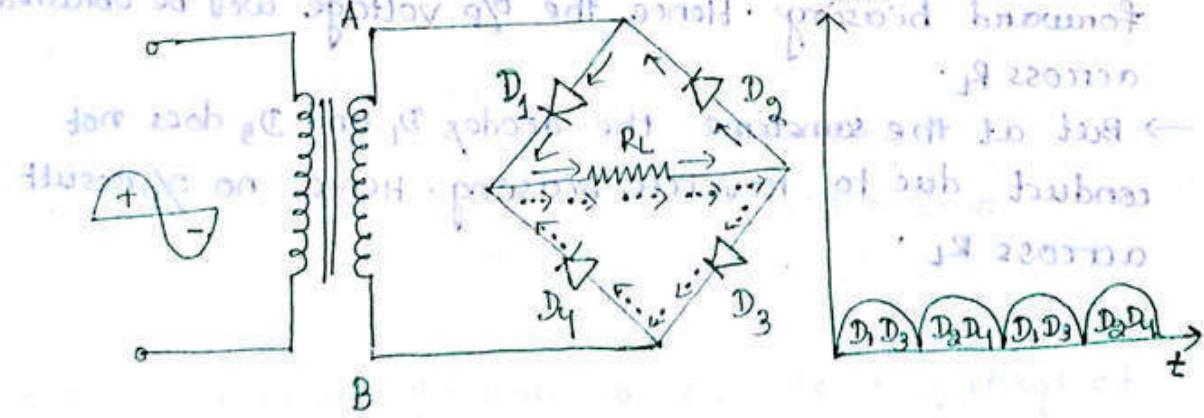

Construction :

- It consists of 4 diodes that D_1 , D_2 , D_3 and D_4 which are connected to form a bridge.
- The ac supply to be rectified is supplied to the diagonally opposite ends of the bridge through the transformer.
- Between other two ends of the bridge, the load resistor R_L is connected.

Working :

During +ve halfcycle of ac :

- During the +ve halfcycle of secondary voltage, the end 'A' of the secondary winding becomes +ve w.r.t. other end 'B'.
- Now the diodes D_1 and D_3 are forward biased and hence the conventional current flows through the circuit across the R_L .

As a result the o/p voltage will be obtained across R_L .

- But at the same time the diodes D_2 and D_4 does not conduct due to reverse biasing. Hence no o/p results across R_L .

During -ve halfcycle of ac :

- During -ve halfcycle of secondary voltage, the end A becomes -ve w.r.t. the other end B.
- Now the diodes D_2 and D_4 conduct current due to forward biasing. Hence the o/p voltage will be obtained across R_L .
- But at the same time the diodes D_1 and D_3 does not conduct due to reverse biasing. Hence no o/p result across R_L .

Advantages and disadvantages of rectifiers

Advantage of HWR :

- ↳ No o/p components used since less is no. of stages
- ↳ If we are available with small amplitude c/p signal we don't require transformer.

Disadvantages of HWR:

- ↳ The efficiency is very low for HWR (40.5%)

Advantages of FWCR:

- ↳ The o/p can be seen for the full input cycle.
- ↳ Efficiency is high (81%)

Disadvantages of FWCR:

- ↳ centretap location is very difficult.
- ↳ peak reverse voltage = $2V_m$.
- ↳ Number of components required are greater than HWR

Advantages of FWBR:

- ↳ Efficiency is very high (81%)
- ↳ If small amplitude input signal is available, transformer is not required.
- ↳ PIV = V_m
- ↳ Circuit design is simple.

Disadvantages of FWBR:

- ↳ Number of components required are greater than HWR and FWCR.

	HWR	FWR
	CT	BT
I _{dc}	I_m/π	$2I_m/\pi$
I _{rms}	$I_m/\sqrt{2}$	$I_m/\sqrt{2}$
PIV	V_m	$2V_m$

	HWR	FWR
	CT	BT
II	40.5%	81%
RF	1.21	0.48

Ripple factor:

- In rectifiers the main objective is dc voltage at the o/p. But in rectifier ckt we do not get exact dc % . The dc o/p is pulsating in nature.

- Some ac components along with dc component can be seen at the o/p.
- Ripple factor is the ratio between rms value of the ac component and dc component.

$$R.F = \frac{\text{rms value of ac component } (I_{ac})}{\text{dc component } (I_{dc})}$$


$$I_{rms}^2 = I_{dc}^2 + I_{ac}^2$$

$$\Rightarrow \frac{I_{rms}^2}{I_{dc}^2} = 1 + \frac{I_{ac}^2}{I_{dc}^2}$$

$$\Rightarrow \frac{I_{rms}^2}{I_{dc}^2} - 1 = \frac{I_{ac}^2}{I_{dc}^2}$$

$$\Rightarrow \left(\frac{I_{ac}}{I_{dc}}\right)^2 = \left(\frac{I_{rms}}{I_{dc}}\right)^2 - 1$$
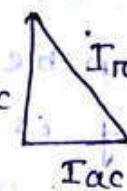
$$\Rightarrow \boxed{\frac{I_{ac}}{I_{dc}} = \sqrt{\left(\frac{I_{rms}}{I_{dc}}\right)^2 - 1}}$$




- Q. An ac supply of 280V is applied to HWR through a transformer of turn ratios 10:1. Find out the
- (1) Output dc voltage
 - (2) DC current

→

$$\boxed{\frac{N_1}{N_2} = \frac{V_1}{V_2} = \frac{I_2}{I_1}}$$

$$\boxed{R_L = 800\Omega}$$

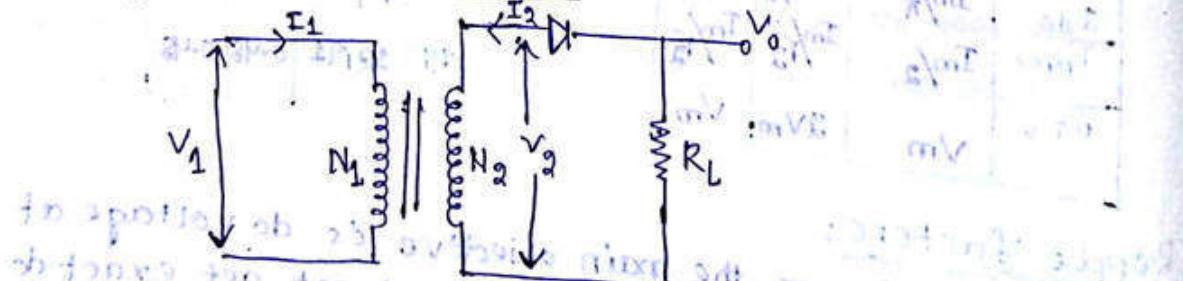


$$V_2 = V_m \quad (\text{HWR})$$

$$V_{rms} = 280 \text{ V}$$

$$V_{rms} = \frac{V_m}{\sqrt{2}}$$

$$\Rightarrow 280 = \frac{V_m}{\sqrt{2}}$$

$$\Rightarrow V_m = 325.26 \text{ (V)}$$

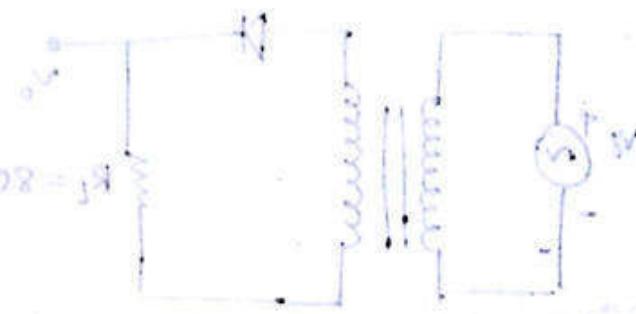

$$\frac{V_1}{V_2} = \frac{N_1}{N_2}$$

$$\Rightarrow \frac{325.26}{V_2} = \frac{10}{1} \Rightarrow V_2 = \frac{325.26}{10} = 32.5 \text{ V}$$

$$I_{dc} = \frac{I_m}{\pi}$$

$$V_{dc} = \frac{V_m}{\pi} = \frac{32.5}{\pi} = 10.34 \text{ V}$$

$$V_o = I_{dc} \times R_L = \frac{10.34}{800} = 0.0128 \text{ A}$$

$$= \frac{I_m}{\pi} \times R_L$$

$$= \frac{V_m}{\pi} = \frac{32.5}{\pi} = 10.34 \text{ V}$$

$$\frac{V_m}{\pi} = \frac{I_m}{\pi} \times R_L$$

$$\Rightarrow 32.5 = I_m \times R_L$$

$$\Rightarrow 32.5 = I_m \times 800$$

$$\Rightarrow I_m = \frac{32.5}{800} = 0.0128 \text{ A}$$


Q. A crystal diode having internal resistance is equal to 20Ω used in HWR. The applied voltage is equal to $50 \text{ sin } \omega t$. The load resistance 800Ω . Find out I_{dc} , I_{rms} , $P_o(\text{dc})$, $P_o(\text{ac})$, n ($r_f = 20 \Omega$), η ($r_f = 0 \Omega$)

$$\left(\frac{32.5}{800} \right) = \frac{0.0128 \text{ A}}{800 \Omega}$$

compare two results.

$$V_o = V_{dc} = ?$$

$$P_{dc} = 0$$

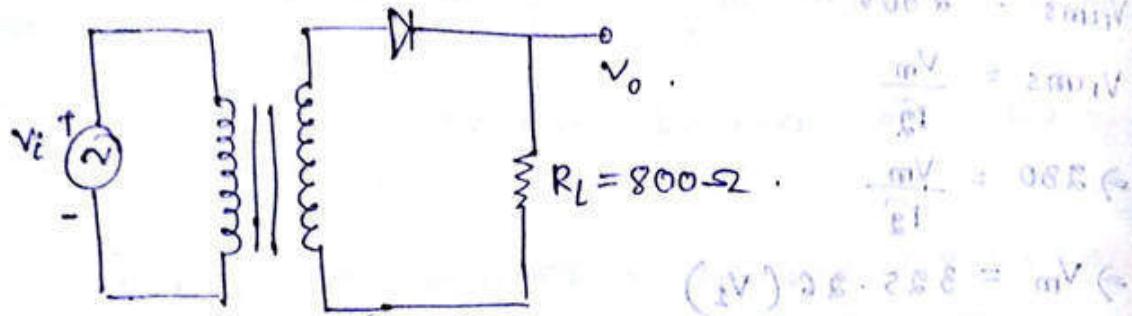

$$V = V_m \sin(\omega t + \phi)$$

$$V = 50 \sin \omega t$$

$$V_m = 50$$

$$V_0 = V_{dc} = \frac{V_m}{\pi} = \frac{50}{\pi} = 15.91 V$$

$$I_{dc} = \frac{V_0}{R_L + r_f} = \frac{15.91}{800} = 0.019 A$$

$$I_m = \frac{V_m}{R_L + r_f} = \frac{50}{800} = 0.0625 A$$

$$I_{rms} = \frac{I_m}{2} = \frac{0.0625}{2} = 0.03125 A$$

$$P_{dc} = I_{dc}^2 \times R_L = (0.019)^2 \times 800 = 0.2888$$

$$P_{ac} = I_{rms}^2 \times (R_L + r_f) = (0.03125)^2 \times 800 = 0.75781125$$

$$\eta = \frac{I_{dc}^2 \times R_L}{I_{rms}^2 (R_L + r_f)}$$

$$= \frac{(0.019)^2 \times 800}{(0.03125)^2 (800 + 20)} = \frac{0.2888}{0.75781125} = 0.3810$$

$$\eta = \frac{I_{dc}^2 \times R_L}{I_{rms}^2 (R_L + r_f)} = \frac{I_{dc}^2 \times R_L}{I_{rms}^2 \times R_L} = \left(\frac{I_{dc}}{I_{rms}} \right)^2$$

$$= \left(\frac{0.019}{0.03125} \right)^2 = 0.390$$

$$= 39\%$$

$$6. I_s = 10^{-10} A$$

$$\eta = 2$$

$$V_D = 0.65 V$$

$$I_D = ?$$

$$\rightarrow V_T = \frac{kT}{q} = \frac{kT}{e} = \left(\frac{k}{q}\right) \times T = 0.02585 \approx 0.026 V \approx 26 mV$$

$$(\because k = 1.38 \times 10^{-23} J/K)$$

$$I_D = I_s (e^{V_D/nV_T} - 1)$$

$$\begin{aligned} \Rightarrow \ln I_D &= \ln \{ I_s (e^{V_D/nV_T} - 1) \} \\ &= \ln \{ I_s e^{V_D/nV_T} - I_s \} = 26 mV - 26 mV \\ &= \frac{\ln (I_s e^{V_D/nV_T})}{\ln I_s} = \frac{\ln I_s + \ln e^{V_D/nV_T}}{\ln I_s} \\ &= \frac{\ln I_s + \frac{V_D/nV_T (\ln e)}{\ln I_s}}{\ln I_s} \\ &= 1 + \frac{V_D/nV_T}{\ln I_s} = 1 + \frac{0.65}{0.026} = 1.25 \end{aligned}$$

LectureNotes.in

$$Lect = 1 + \frac{0.65}{0.026} \times \frac{1}{-10}$$

$$= 1 - \frac{0.65}{0.52} =$$

$$= -0.25$$

$$I_D = e^{-0.25} = 0.77 A$$

Q For FWR the o/p $R_L = 2000\Omega$. The forward resistance $r_{cf} = 1000\Omega$. It has infinite backwarded resistance. The rms value of transformer secondary voltage from mid point to each terminal = 250V. Find I_{dc} , I_{rms} , P_{out} , efficiency, input ac power.

$$\rightarrow \text{input ac power: } P_{in} = \frac{V_m^2}{R_L + r_{cf}} = \frac{V_m^2}{2000 + 1000} = \frac{V_m^2}{3000}$$

$$R_L = 2000\Omega$$

$$r_{cf} = 1000\Omega$$

$$V_{rms} = 250V$$

$$V_{rms} = \frac{V_m}{\sqrt{2}}$$

$$\rightarrow V_m = V_{rms} \sqrt{2} = 250\sqrt{2}V$$

$$I_m = \frac{V_m}{R_L + r_{cf}} = \frac{250\sqrt{2}}{3000} = 0.1178A$$

$$I_{rms} = \frac{I_m}{\sqrt{2}} = \frac{0.1178}{\sqrt{2}} = 0.083A$$

$$I_{dc} = \frac{2I_m}{\pi} = \frac{2 \times 0.1178}{\pi} = 0.0749A$$

$$P_{ac} = I_{rms}^2 \times (R_L + r_{cf})$$

$$= 20.667$$


$$P_{dc} = I_{dc}^2 \times R_L$$

$$= (0.0749)^2 \times 2000$$

$$= 11.220$$

$$\eta = \frac{P_{dc}}{P_{ac}} = \frac{11.220}{20.667} = 0.5428$$

$$= 54.28\%$$

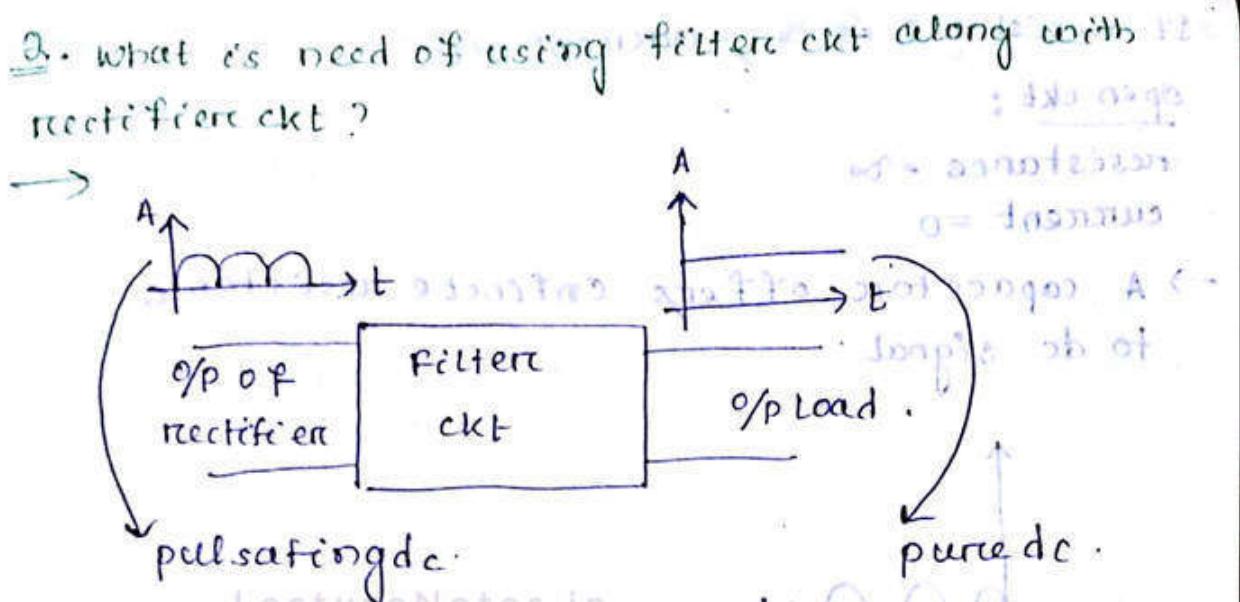


- The o/p of the rectifier is pulsating and contains a steady dc component with undesirable ripples.
- If such a pulsating dc is given to electronic ckt, it produces ham (disturbance).
- Therefore the ac component or ripples have to kept away from the load (electronic ckt). This is achieved by using filter ckt.

- Q. what are the components used in filter ckt?
- \hookrightarrow capacitor
 - \hookrightarrow inductor

Capacitive Reactance:

The resistance offered by the capacitor to the flow of current is called capacitive reactance and is represented with X_C .
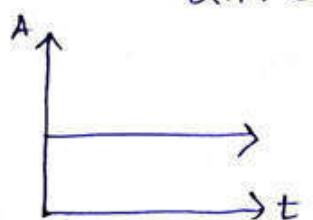
$$X_C = \frac{1}{2\pi f C} = \frac{1}{\omega C}$$



Frequency of dc = 0.

$$\text{so } X_C = \frac{1}{2\pi \times 0 \times C} = \frac{1}{0} = \infty \Omega$$



If resistance is ∞ , current = 0

open ckt:

resistance = ∞

current = 0

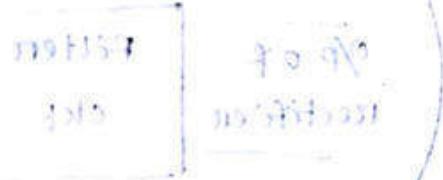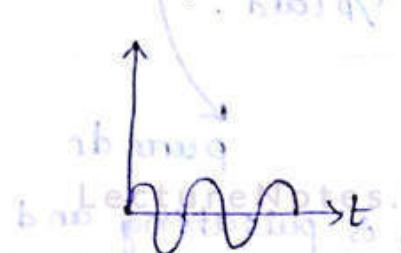→ A capacitor offers infinite resistance to dc signal.



shunting

* When the frequency $f = f_0$ (when phase is 90°)

$$X_C = \frac{1}{2\pi f C} = k\Omega$$

→ $k\Omega$ \rightarrow shunting value

Inductive Reactance (X_L):

The resistance offered by the conductors to the flow of current is known as inductive reactance.

$$X_L = 2\pi f L$$

numbers \rightarrow



LectureNotes.PDF (Page 9)

$$X_L = 2\pi \times 0 \times L = 0 \Omega$$


$$\rightarrow I R = 0 \Omega \rightarrow I$$



On the $I-V$ graph

$$V = -jI \times Z = -jI \times 0 \Omega$$

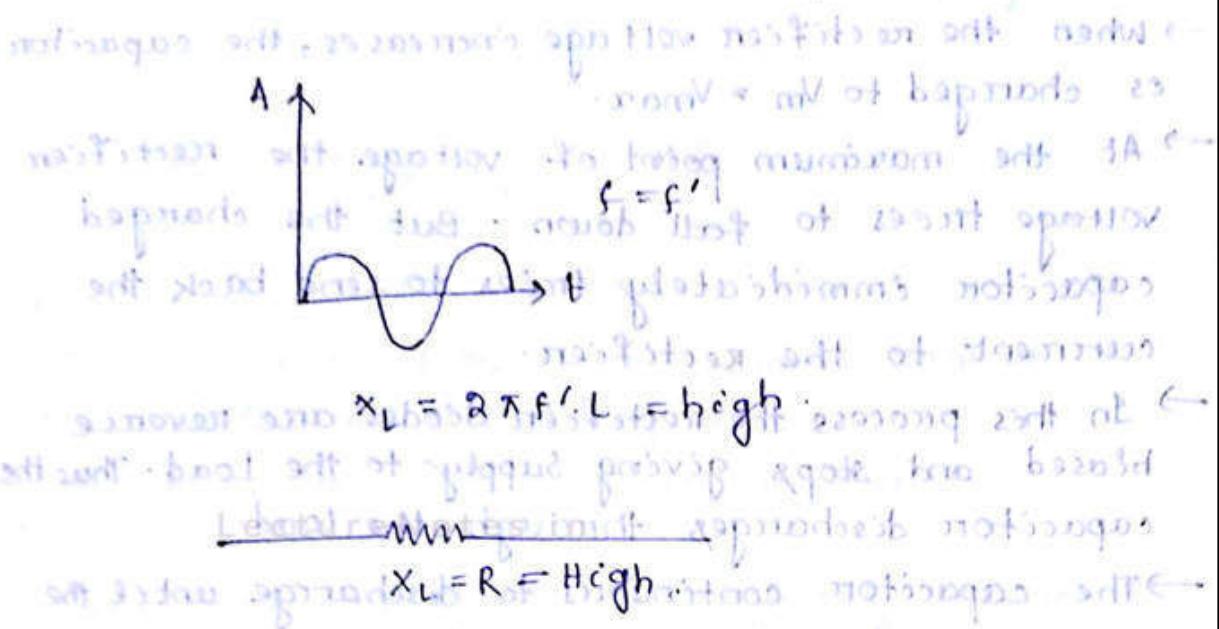→ The inductor allows the flow of dc signal through.



- The inductor offers a very high resistance to the flow of ac signal.
- A capacitor is connected parallel to the ckt in such a manner that it bypasses the ac component and blocks the dc component.
- An inductor is connected in series with the ckt in such a manner that it blocks the ac component and gives the easy path to dc component.

Types of filter ckt:

- ↳ i) capacitive / shunt
- ↳ ii) Inductive / series
- ↳ iii) Lc type / choke type
- ↳ iv) π type / c/p capacitor


capacitive shunt filter:

- In this case a capacitor of very large value is just connected across the o/p terminal or in parallel to the o/p load i.e. why it is called shunt capacitor filter.
- The capacitor offers a low reactive path to the ac signal and acts as an open ckt for dc signal, all of the dc signal reaches at the low terminal with ac signal bypasses to ground.


Working principle

- When the rectifier voltage increases, the capacitor is charged to $V_m = V_{max}$.
- At the maximum point of voltage, the rectifier voltage tries to fall down. But the charged capacitor immediately tries to send back the current to the rectifier.
- In this process the rectifier diodes are reverse biased and stops giving supply to the load. Thus the capacitor discharges through the load.
- The capacitor continues to discharge until the source voltage is more than the capacitor voltage and the capacitor is again charged peak value V_m .
- During this time the rectifier supplies the charging current I_c and the load current I_L .
- The smoothness of O/P voltage depends upon the time constant.
- The longer the time period, the steadiness of the O/P voltage.
- This can be achieve by using a large value of capacitor.

Filter ckt

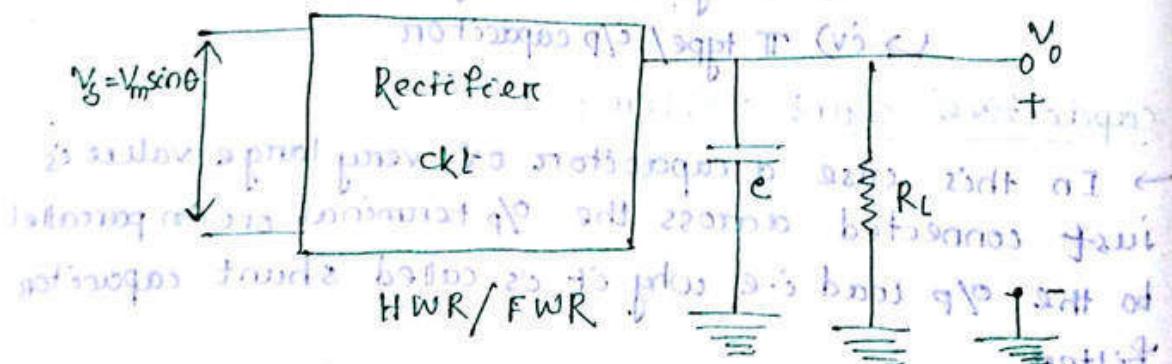

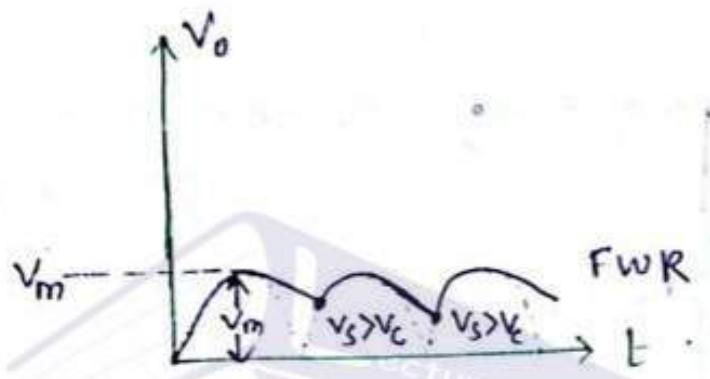This diagram illustrates the basic working principle of a half-wave rectifier with a filter circuit. The AC source provides the input voltage, which is rectified by the diode. The resulting DC voltage is then smoothed by the capacitor C and resistor R_L combination to produce a relatively smooth output voltage V_o .



Advantages:

- The magnitude of o/p dc is improved because of the charging and discharging concept.
- It can be applied to both HWR and FWR.

Disadvantages:

- Since capacitor itself draws heavy amount of current from the rectifier, the load current available at the load is very small.

clippers and clampers:

clippers:

- cut off unwanted's as portion having n anti
- negative Lecature Notes. below a to short after gain

clippers

series clipper


biased series

parallel clipper

biased parallel


→ A clipper is an electronic ckt which remove or clips off the ^{un}wanted portion of the c/p signal.

Ex

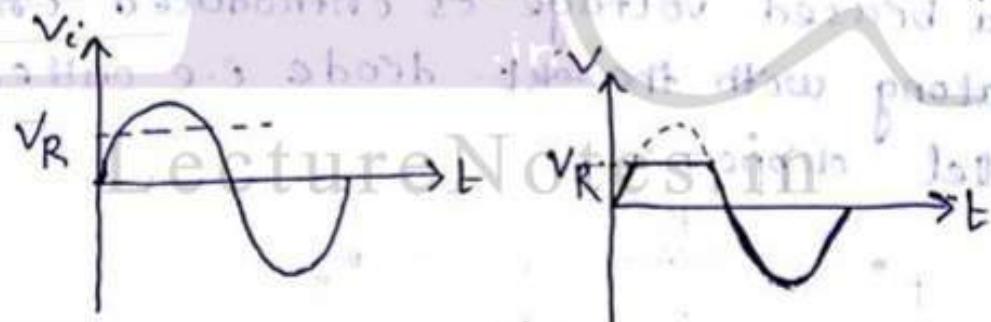


series clipper:

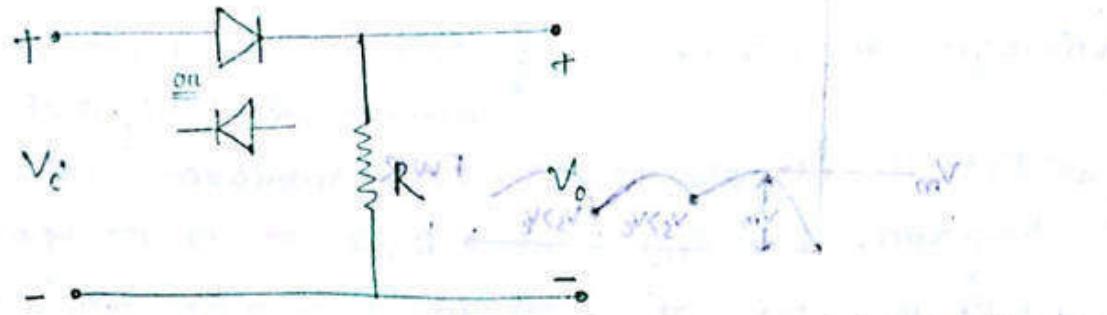when a diode is connected in series with the o/p, it's called series clipper.




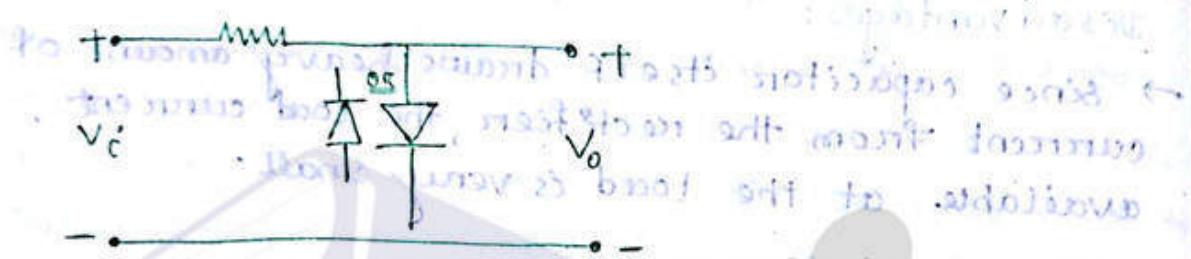Parallel clipper: When a diode is connected in parallel with the op, it is called parallel clipper or bridge clipper.




Biased series clipper:

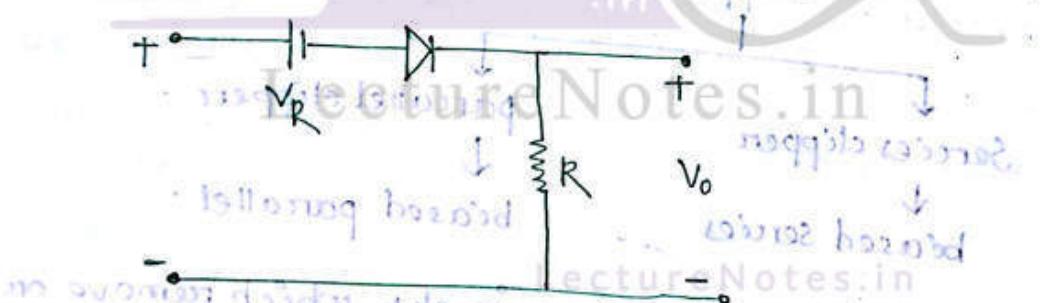When a biased voltage is introduced in the series ckt along with diode i.e. called biased series clipper.







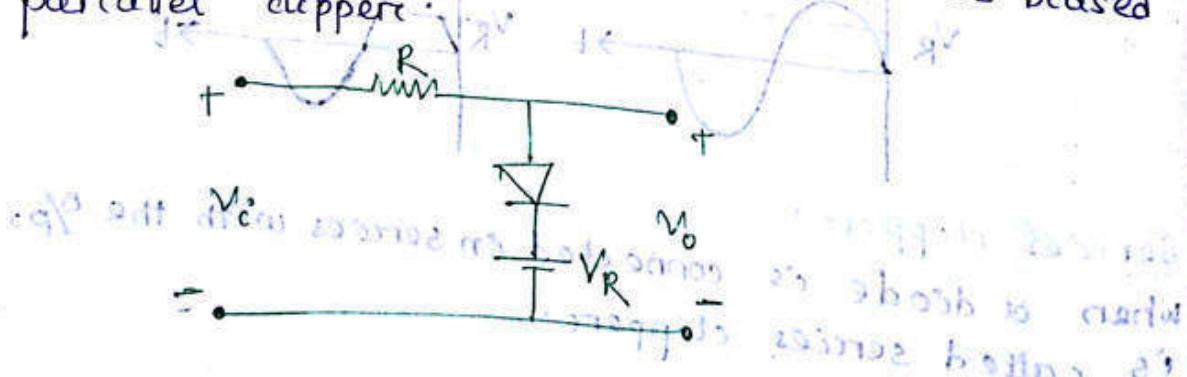
Biased parallel clipper: When a biased voltage is introduced in the parallel ckt along with the op diode i.e. called biased parallel clipper.




Voltage transfer characteristics (VTC):

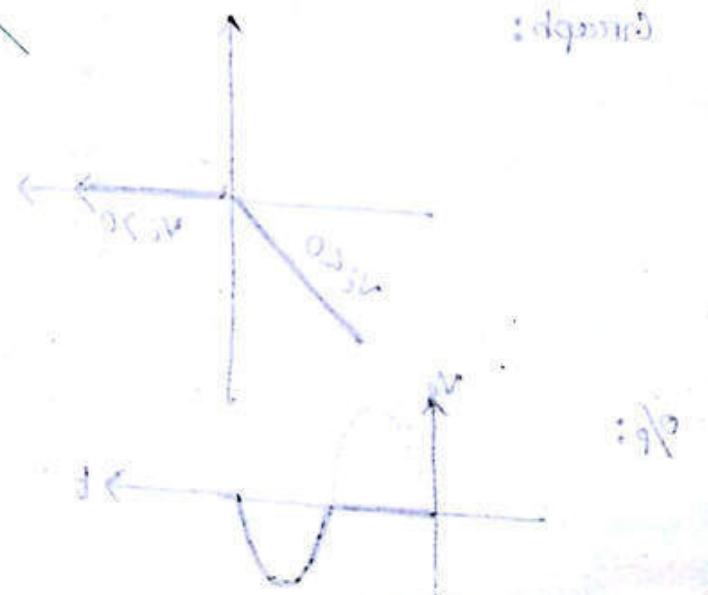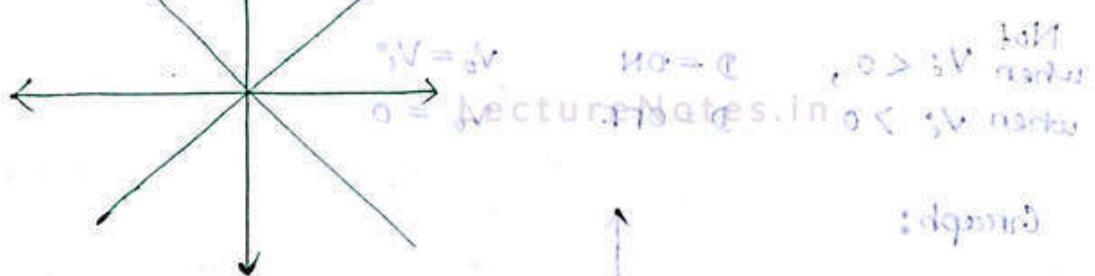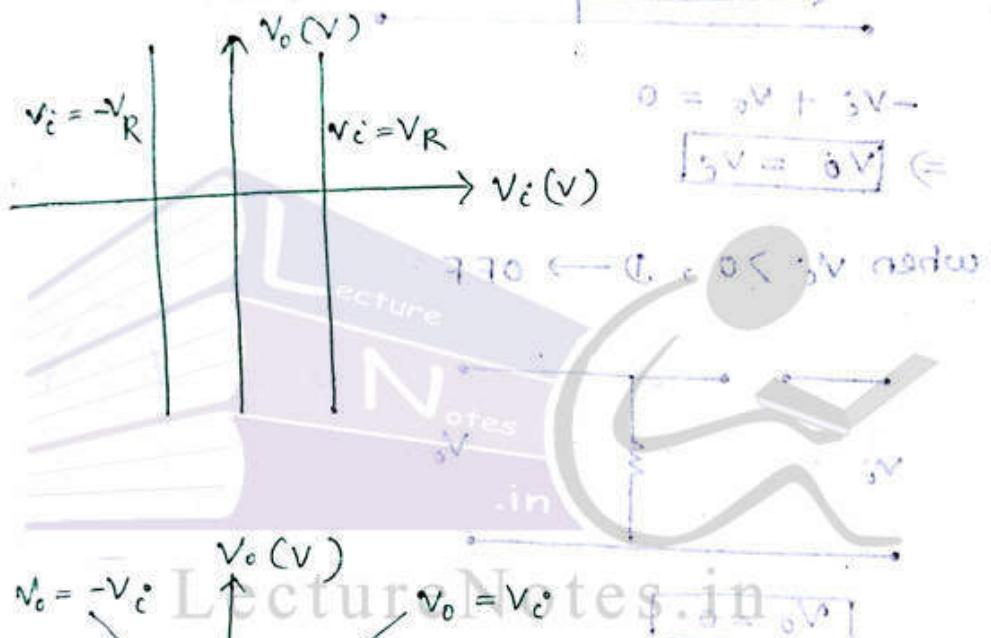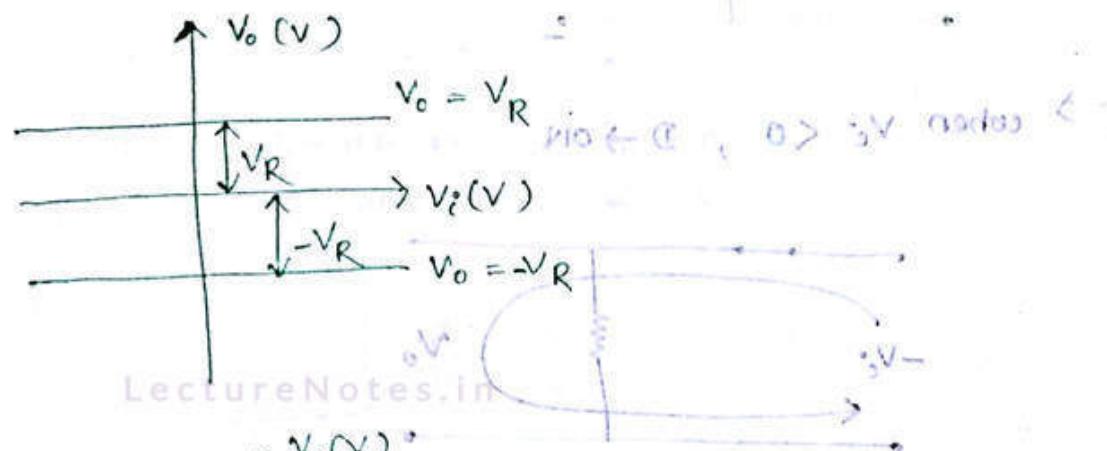→ It is the characteristic graph between o/p voltage and i/p voltage.



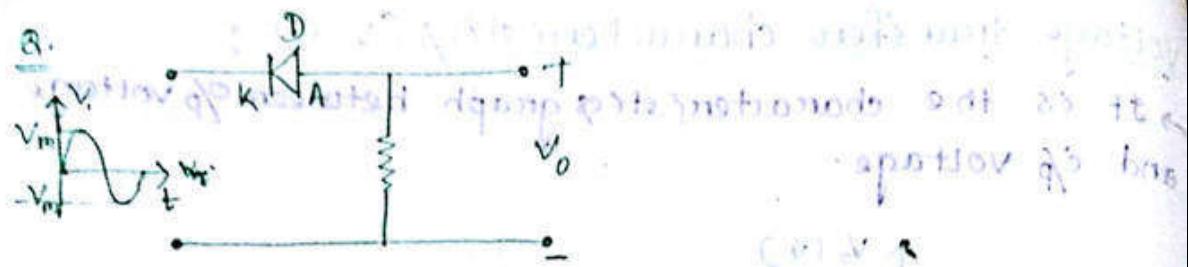

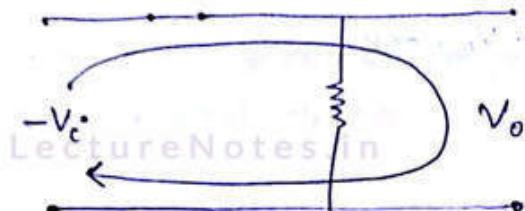
\rightarrow when $V_c < 0$, $D \rightarrow \text{ON}$



$$-V_c + V_o = 0$$

$$\Rightarrow V_o = V_c$$

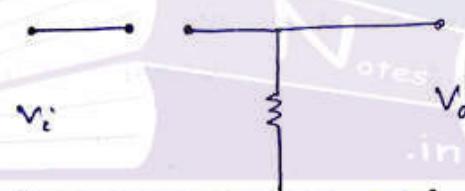when $V_c > 0$, $D \rightarrow \text{OFF}$





$$V_o = 0$$

when $V_c < 0$, $D = \text{ON}$ $V_o = V_c$

when $V_c > 0$, $D = \text{OFF}$ $V_o = 0$



Graph:

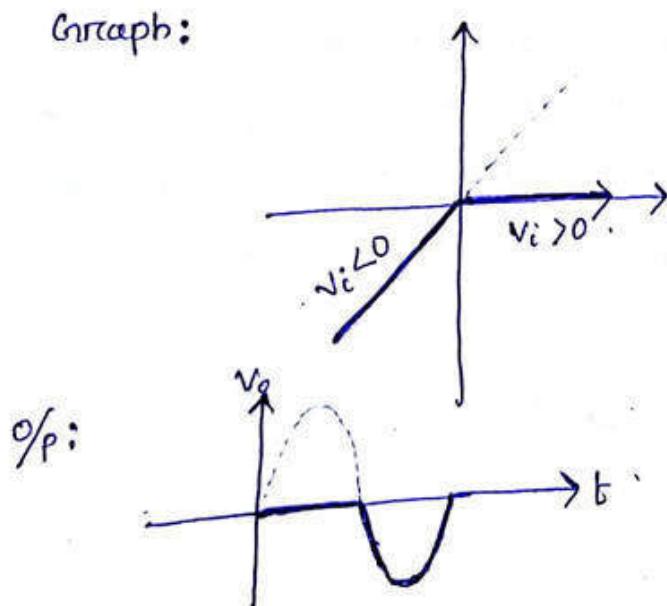

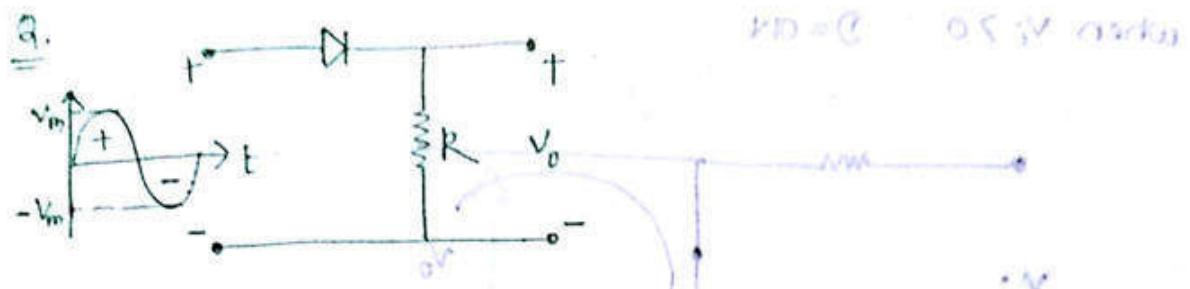


$\rightarrow v_i < 0 \quad D = \text{OFF}(\text{RB}) \quad v_o = 0$

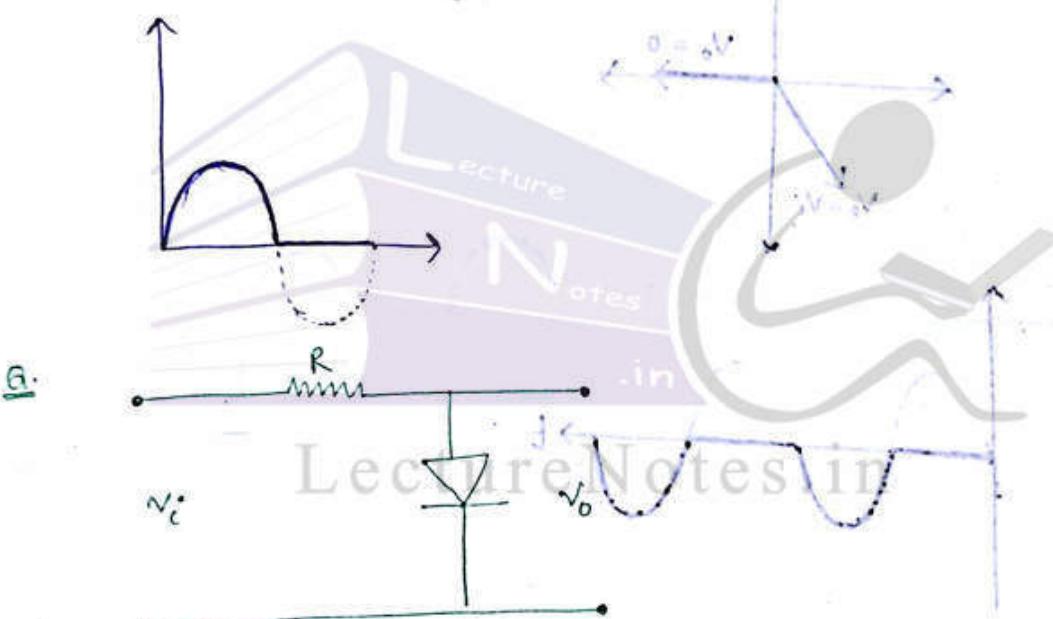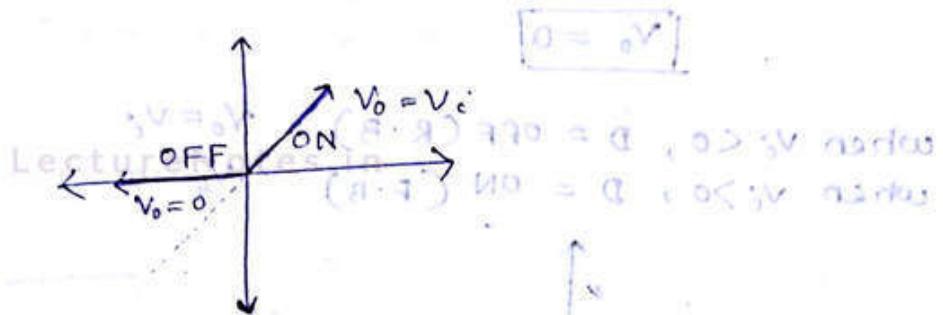$v_i > 0 \quad D = \text{ON}(\text{FB}) \quad v_o = v_i$



$\rightarrow \text{when } v_i < 0 \quad D = \text{OFF}(\text{RB}) \quad v_o = 0$

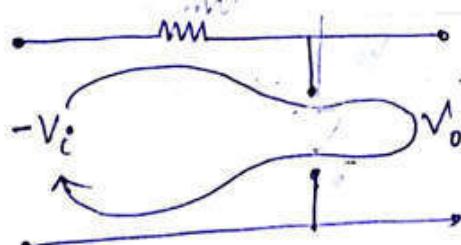
$\text{when } v_i > 0 \quad D = \text{ON}(\text{FB}) \quad v_o = v_i$



$$v_o - v_i = 0$$

$$\Rightarrow v_o = v_i$$

when $V_i > 0$: D = ON

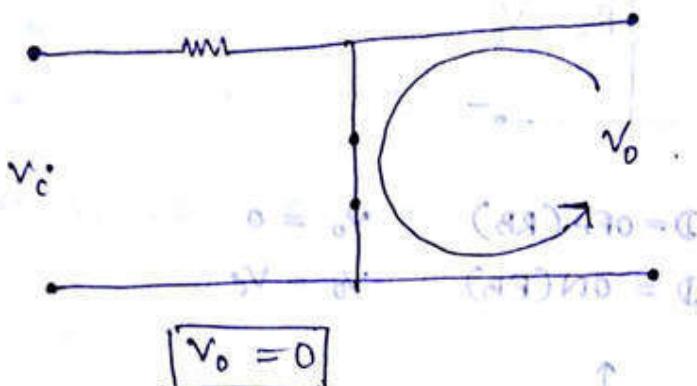


when $V_i < 0$, D = OFF (R · B)


when $V_i > 0$, D = ON (F · B)

$$V_o = V_i$$

$$V_o = 0$$

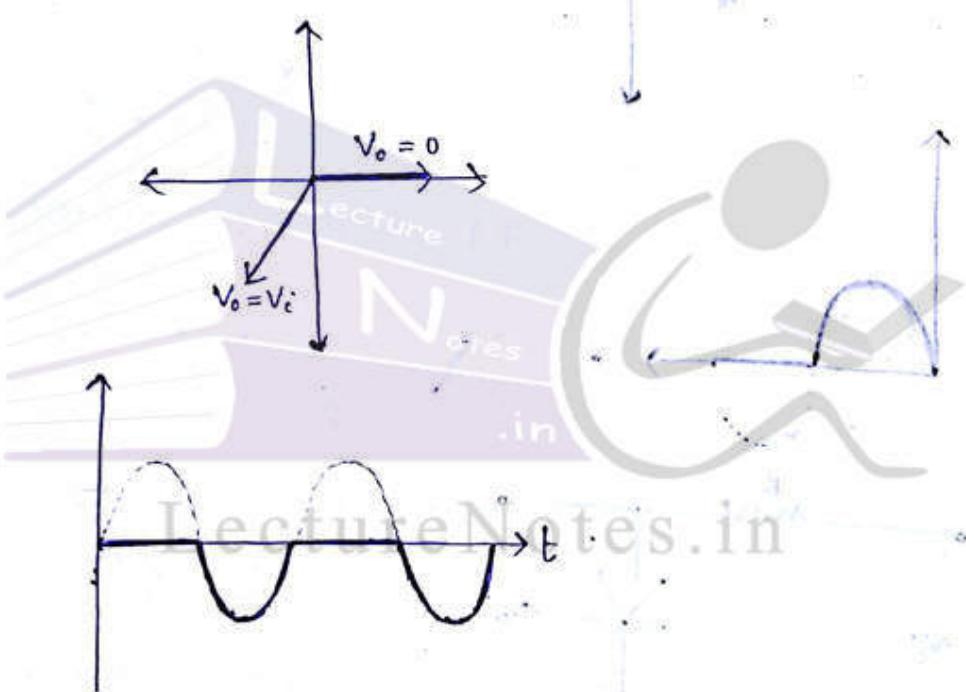


Q.

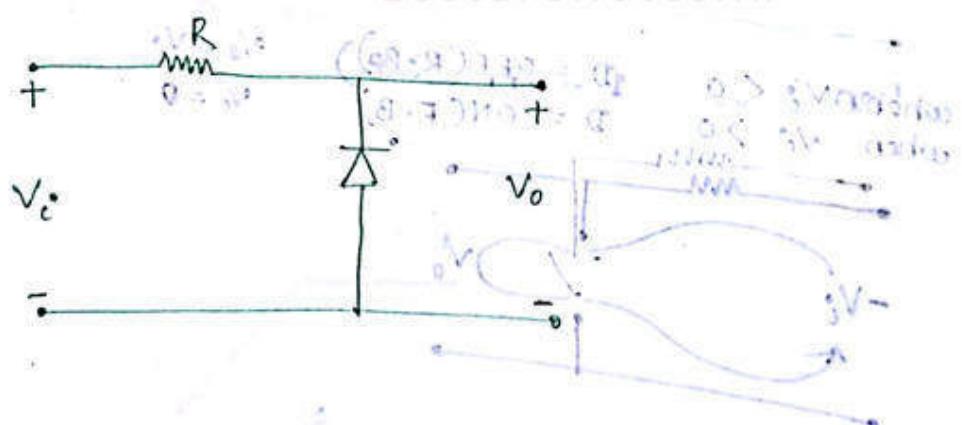


$$D = 3V - 0.2V$$


→

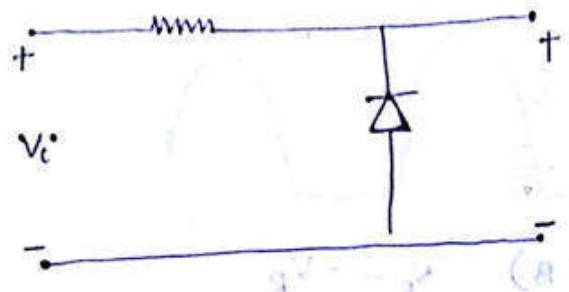

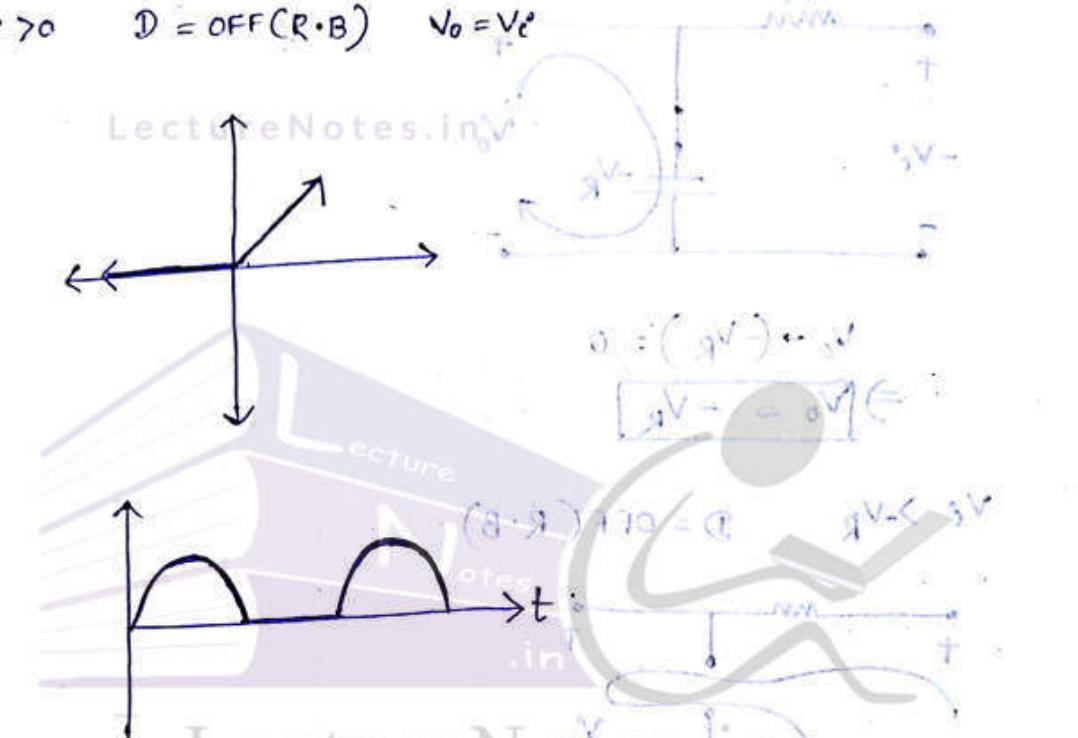$V_i < 0 \quad D = ON(F.B) \quad V_o = 0$
 $V_i > 0 \quad D = OFF(R.B) \quad V_o = V_i$



*

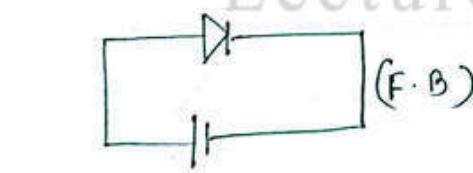


-3V \rightarrow 0V (R.B)

2V \rightarrow 0V (F.B)

-2V \rightarrow -3V (F.B)

?

Q.

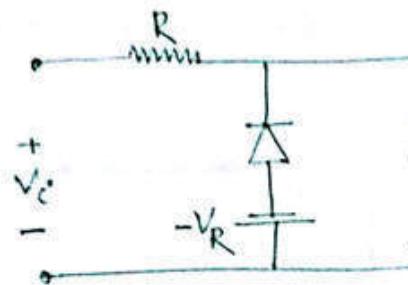


$$\rightarrow V_i < -V_R \quad D = \text{ON} (F \cdot B)$$

$$V_o = -V_R$$

$$0 > 5V \quad (8.1) \text{ NO } = 0 \quad 0 > 5V$$


$$(8.2) \text{ NO } = 0 \quad 0 < 5V$$

$$(8.3) \text{ NO } = 0 \quad 0 < 5V$$

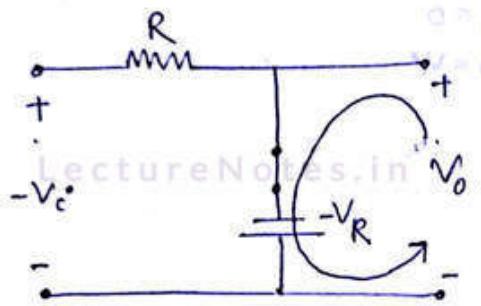






$$\Rightarrow V_o = -V_R$$
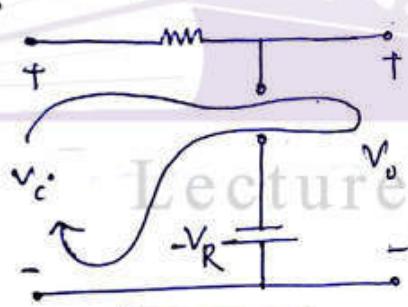
$$V_i > -V_R \quad D = \text{OFF} (R \cdot B)$$




$$V_o = V_i$$

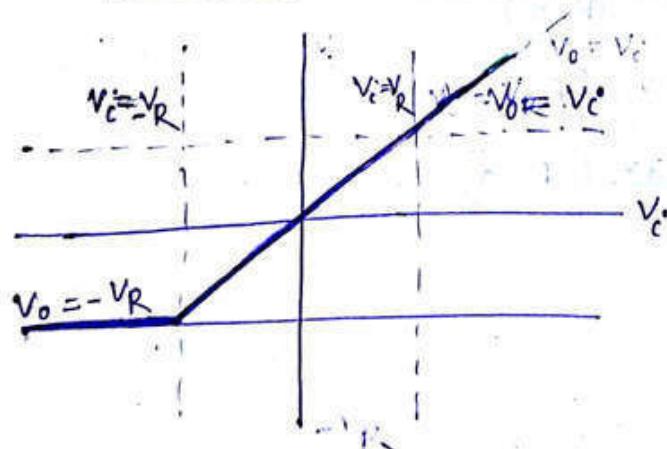

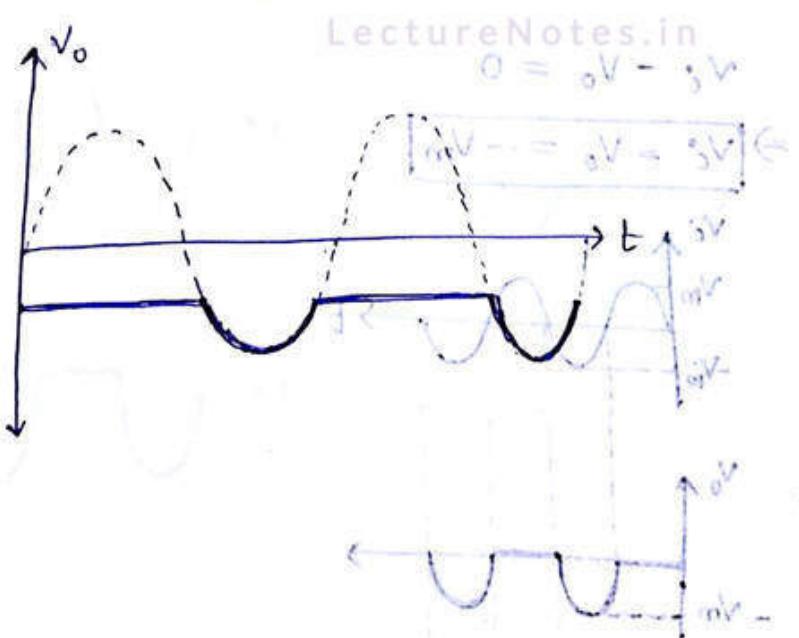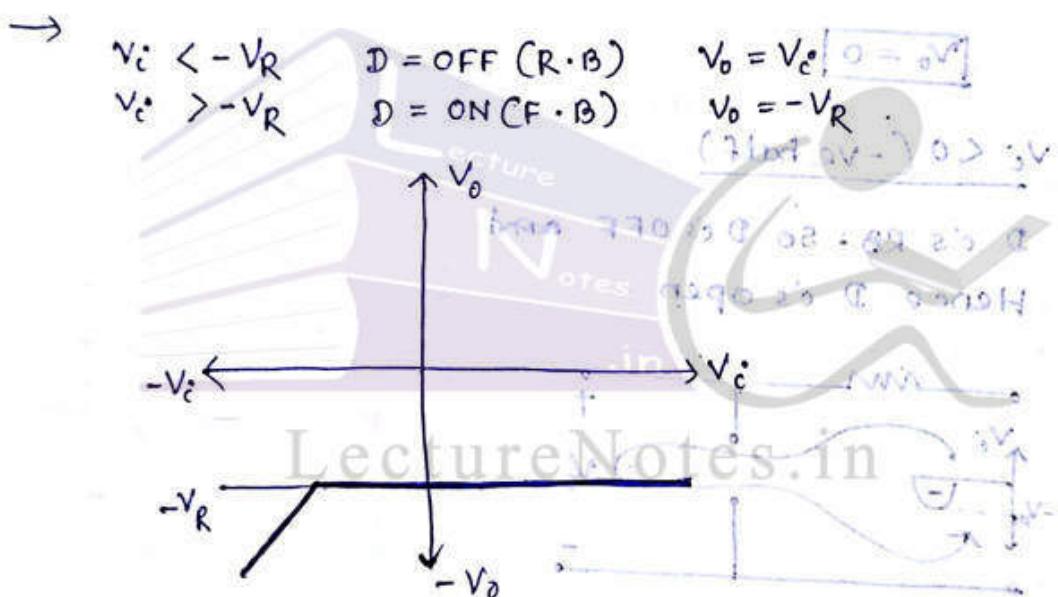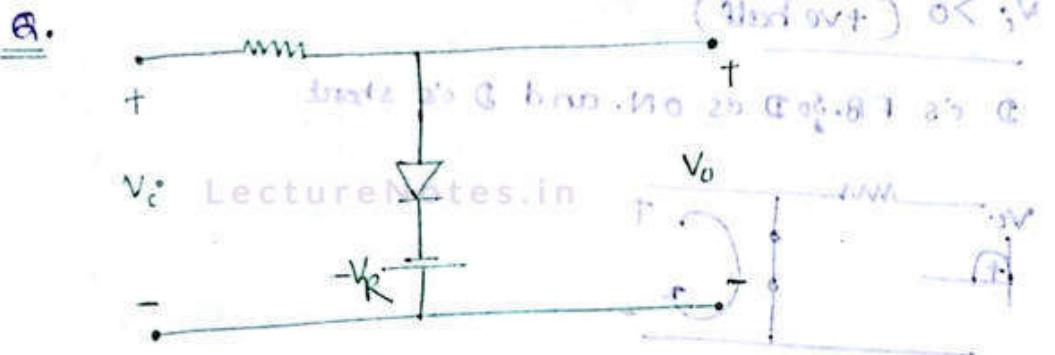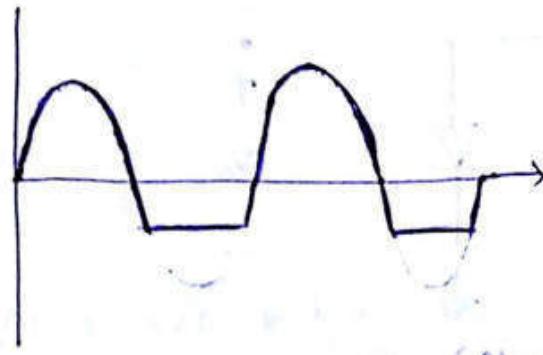


Q.

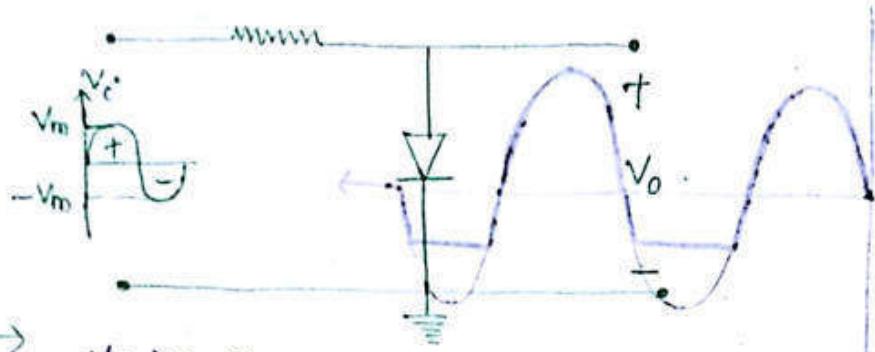

$$\rightarrow \underline{v_i > 0 \text{ (+ve half)}}$$

D c's FB. So D is ON. and D c's short.


LectureNotes.in

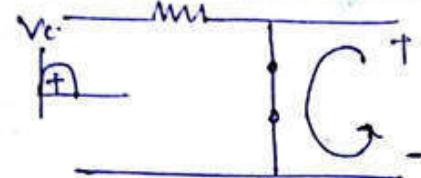

$$\boxed{v_o = 0}$$


$$\underline{v_i < 0 \text{ (-ve half)}}$$

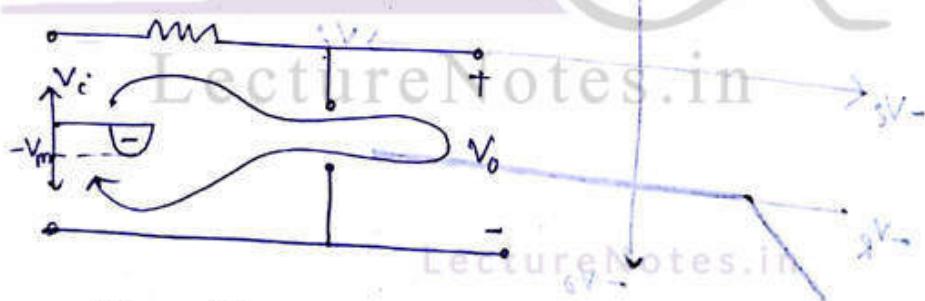
D c's RB. So D c's OFF and
Hence D c's open.



$$v_i - v_o = 0$$

$$\Rightarrow \boxed{v_c = v_o = -v_m}$$

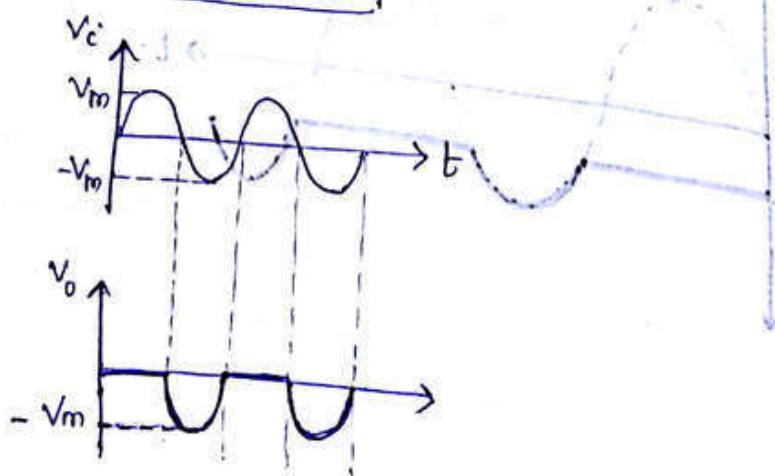


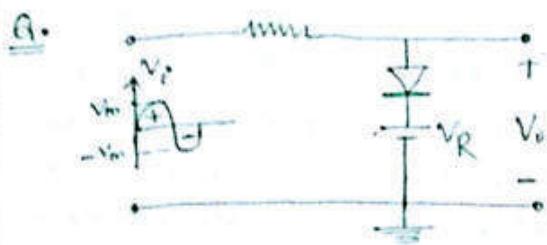

$$\rightarrow V_i > V_R$$

D is FB/D is ON/D is short ckted


$$V_i > V_R \Rightarrow V_R$$

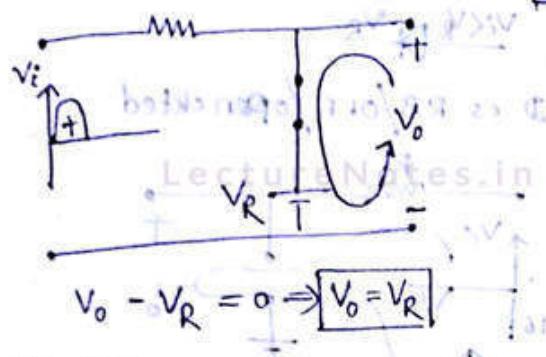


$$V_i < V_R$$

D is RB/D is OFF/D is open ckted



$$V_i < V_R \Rightarrow V_R$$

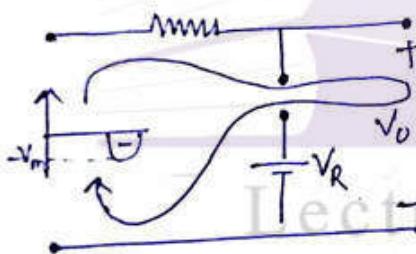


$$V_o = V_i = -V_m$$

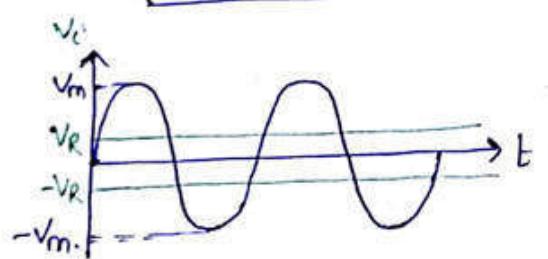

LectureNotes.in

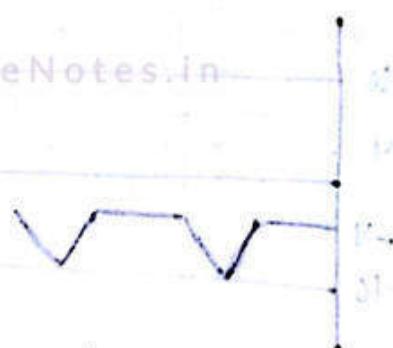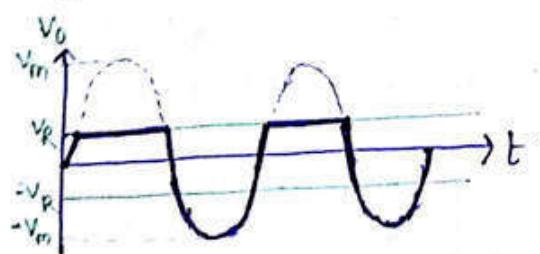



Q.

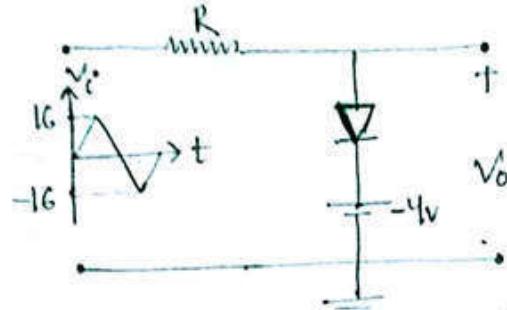

$$\rightarrow v_i > v_R$$

$$v_i > v_R \quad D \text{ is ON}$$


D is FB/ON/shortcirketed

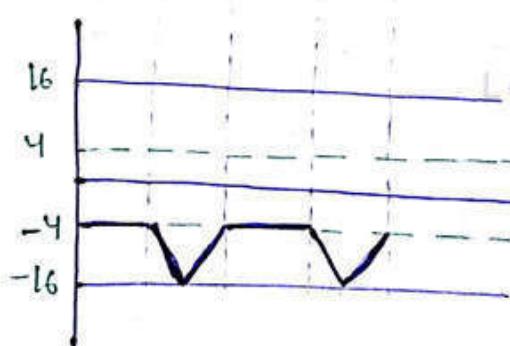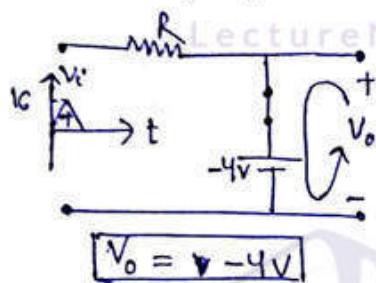

$$v_i < v_R \quad D \text{ is OFF}$$



$$v_i < v_R \quad D \text{ is OFF}$$

D is RB/ON/open cirketed

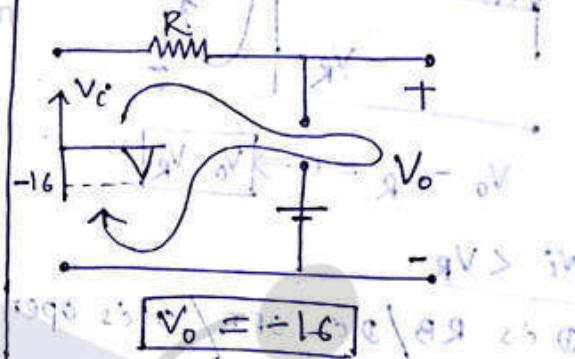

$$v_o = -16V$$


$$16V - 4V = 12V$$

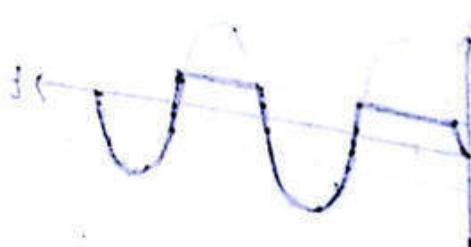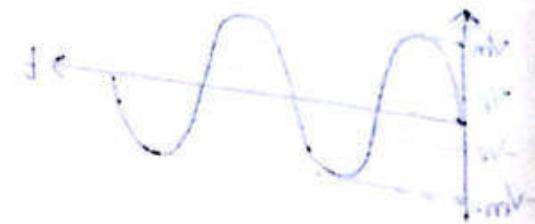

Shortcut Method


- If anode of the diode is connected at the +ve of o/p either of it is series clippers or parallel clippers, +ve part on the above the reference level will be clipped OFF.
- If anode is connected at the -ve of o/p either it is series clippers or parallel clippers, -ve part on the part above reference level will be clipped OFF.

Biased Series Clipper:

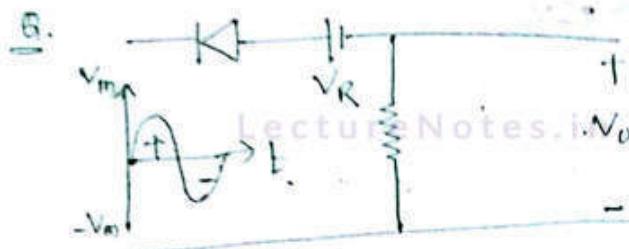

$$\rightarrow V_i < V_R \quad D = ON(F.B) \quad V_o = V_R$$

$$V_i < V_R$$

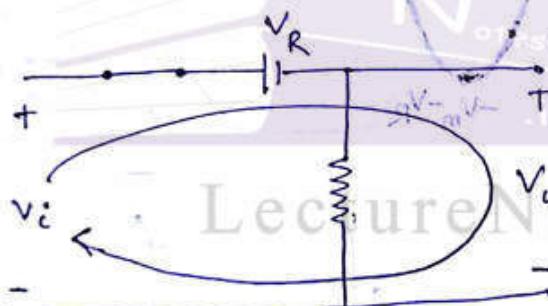

$$V_i - V_R - V_o = 0$$

$$\Rightarrow V_o = V_i - V_R$$


$$\Rightarrow V_o = -V_m - V_R$$

$$V_i > V_R \quad D = OFF(R.B) \quad V_o = 0$$


V_i	V_o
0	$-V_R$
V_R	0
V_m	$V_m - V_R$ (not considered)
$-V_m$	$-V_m - V_R$



$$V_i > V_R$$

D is RB/OFF/open

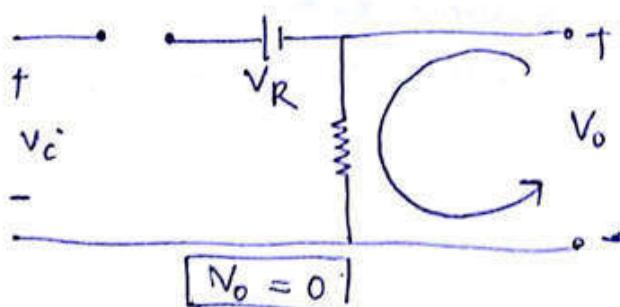






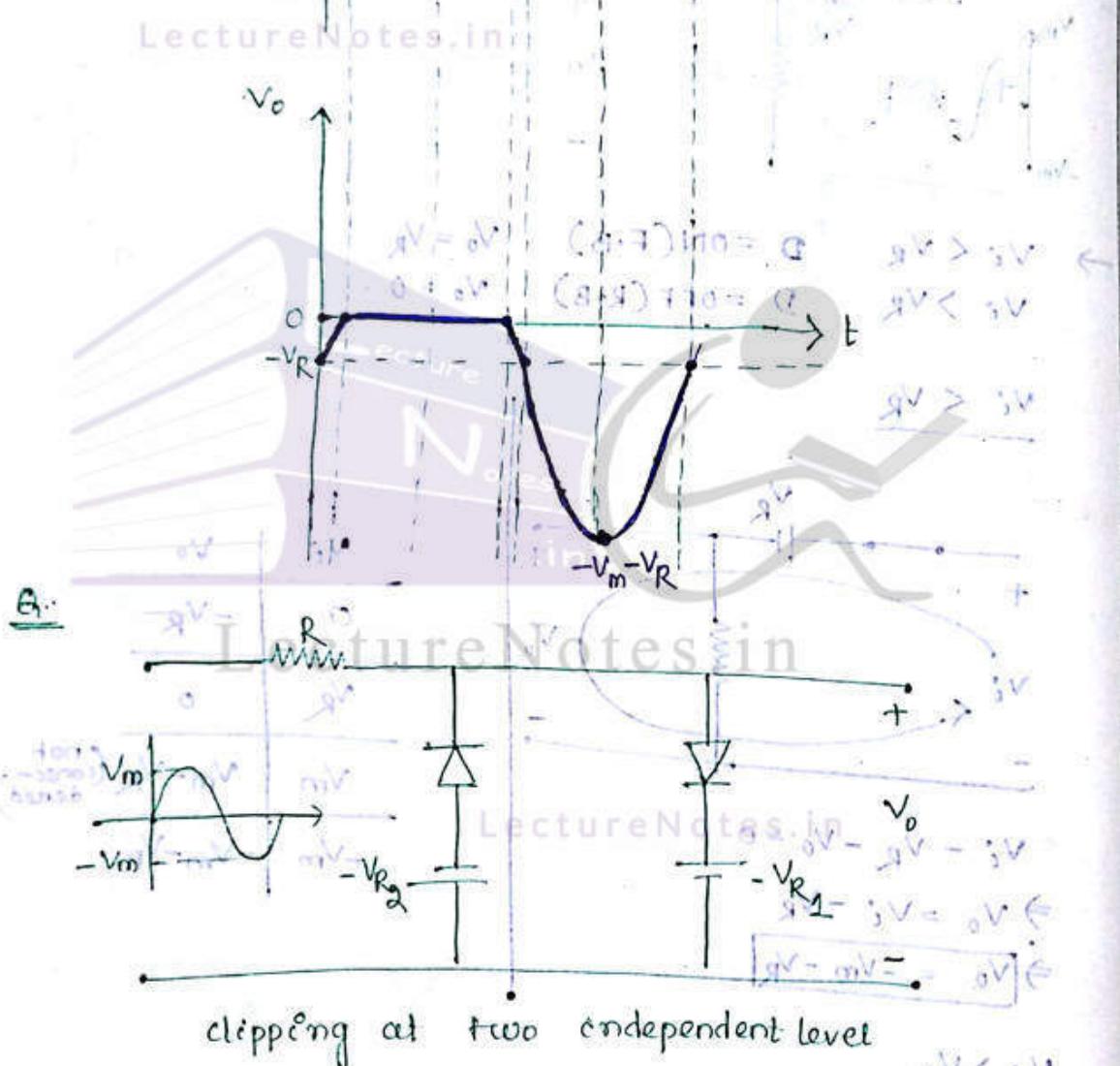
This is the wave form of a sine wave which has been clipped at two levels. The positive half cycle is clipped at level V_R and the negative half cycle is clipped at level $-V_R$. The resulting wave form is shown below.



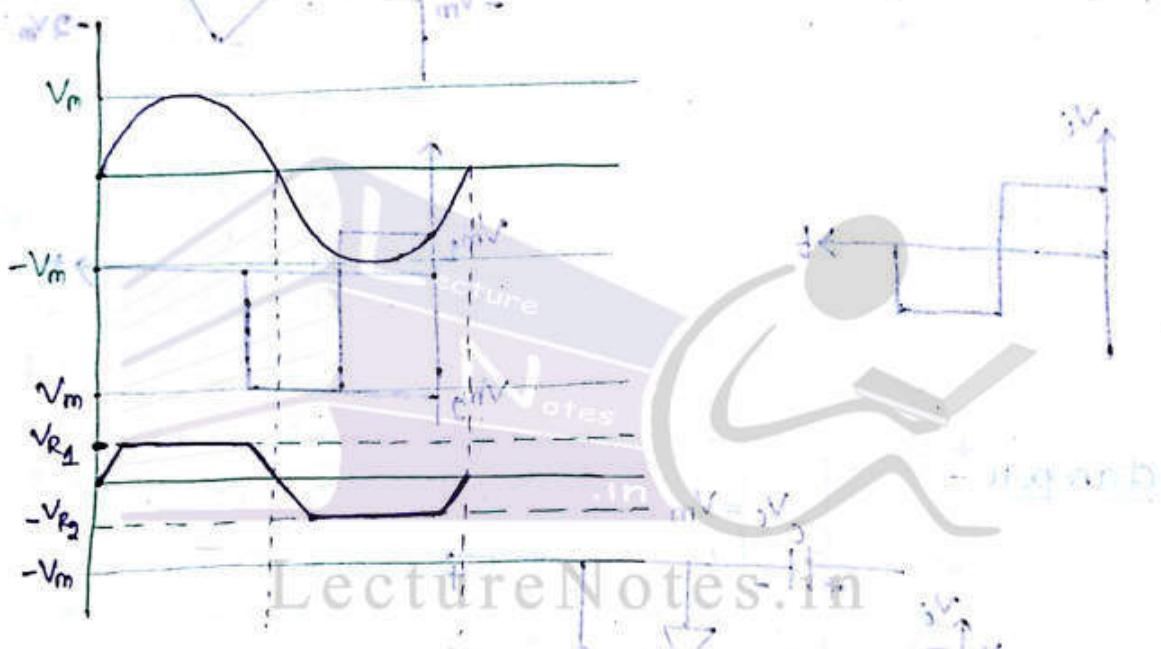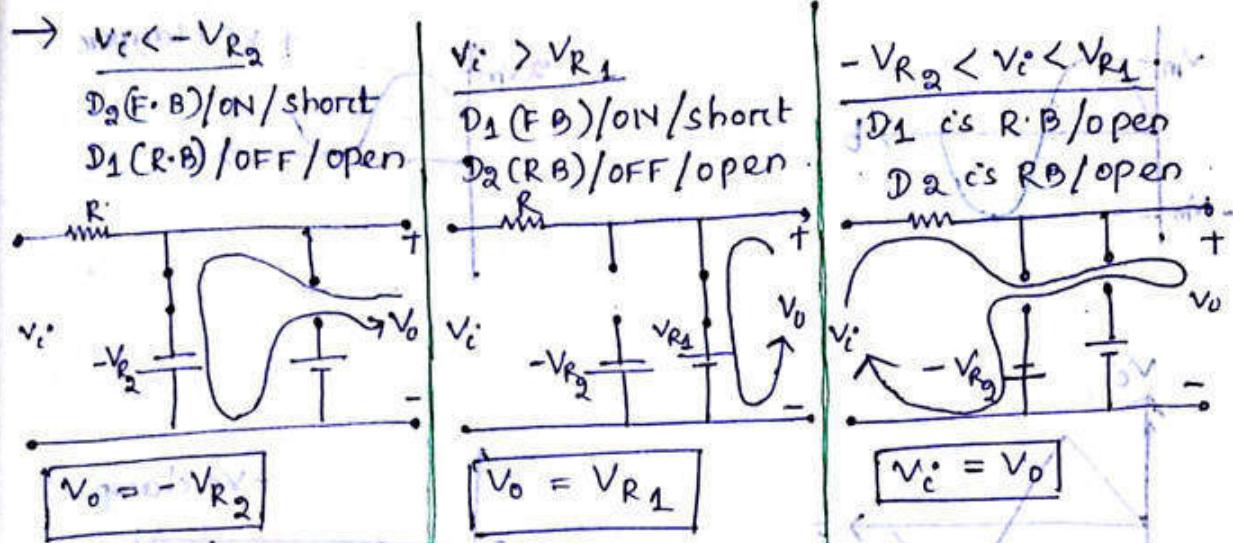


clamper:

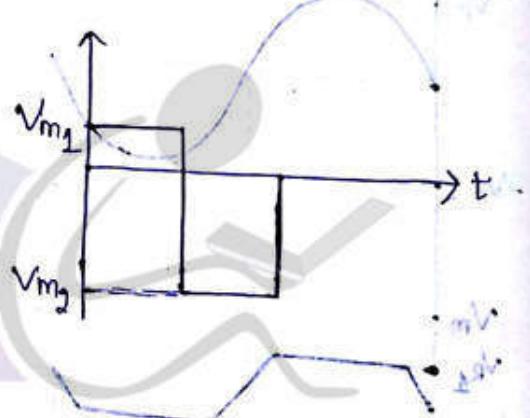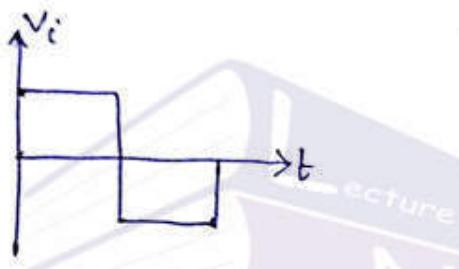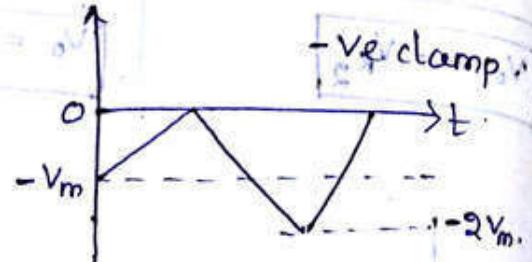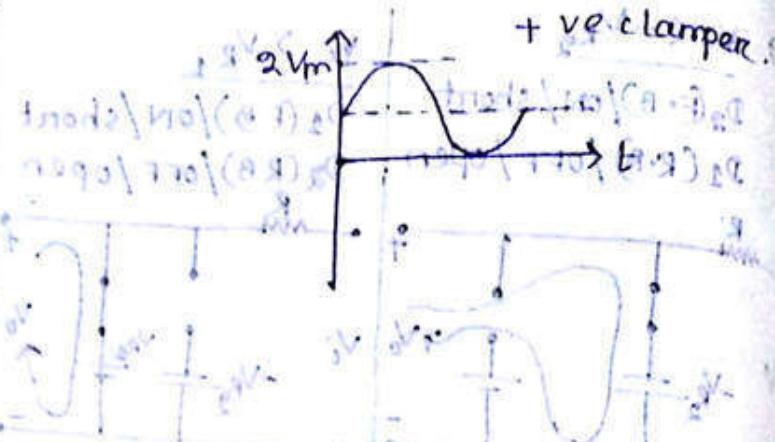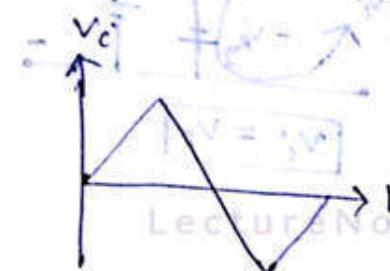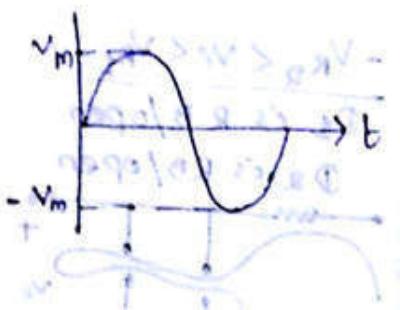- A clamper is an electronic ckt which clamps one fixed the extremities of the c/p signal to a new reference level
- By passing through the clamping ckt the original shape of the c/p signal does not change.
- clamper are of two types.
 - (i) Positive clamper is proposed with $+V_o$ as base with $+V_b$.
 - (ii) Negative clamper is proposed with $-V_o$ as base with $-V_b$.





clamper -

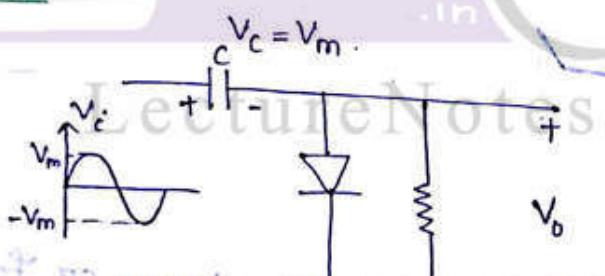


→ During the +ve quarter cycle of i/p signal, the capacitor charges to a maximum value V_m with left + plate +ve and right plate -ve. In this period, diode is forward biased.

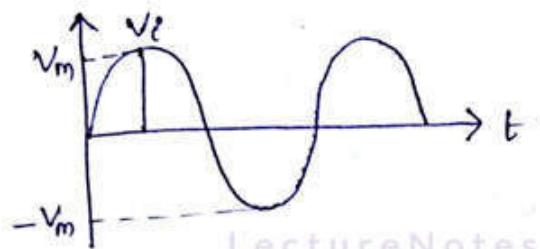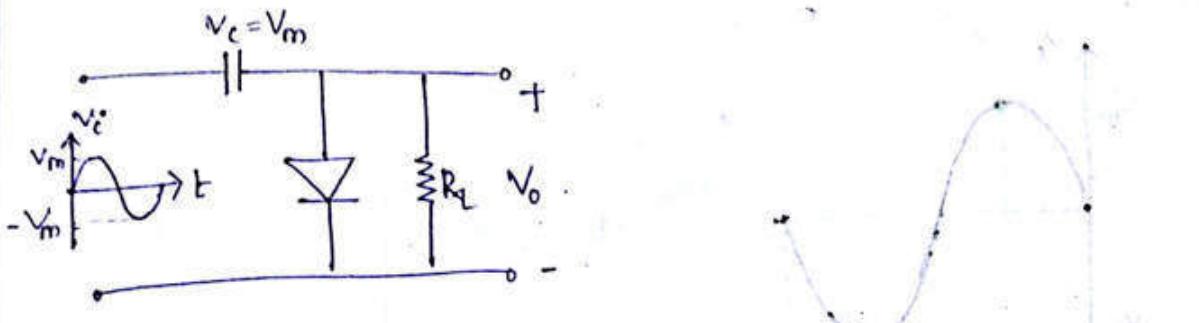→ As the charging time for capacitor is very less than discharging time through load, in the and quarter cycle of the +ve i/p, the capacitor discharges to a negligible value and remains at V_m .



$v_i > 0$

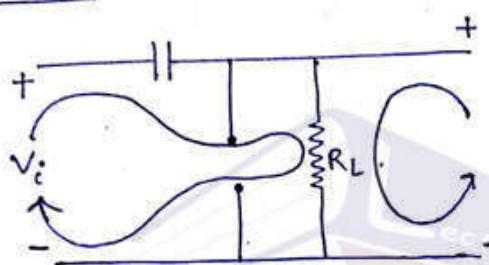

$$1st: v_i - v_c - IR_{L1} = 0$$

$$\Rightarrow v_i - v_c = IR_{L1}$$


$$2nd: v_o - IR_{L1} = 0$$

$$\Rightarrow v_o = IR_{L1}$$

From 1st and 2nd,


$$v_i - v_c = v_o$$

$v_i > 0$

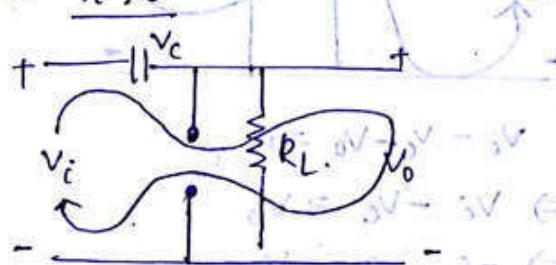

$$v_i - v_c - v_o = 0$$

$$\Rightarrow v_o = v_i - v_c$$

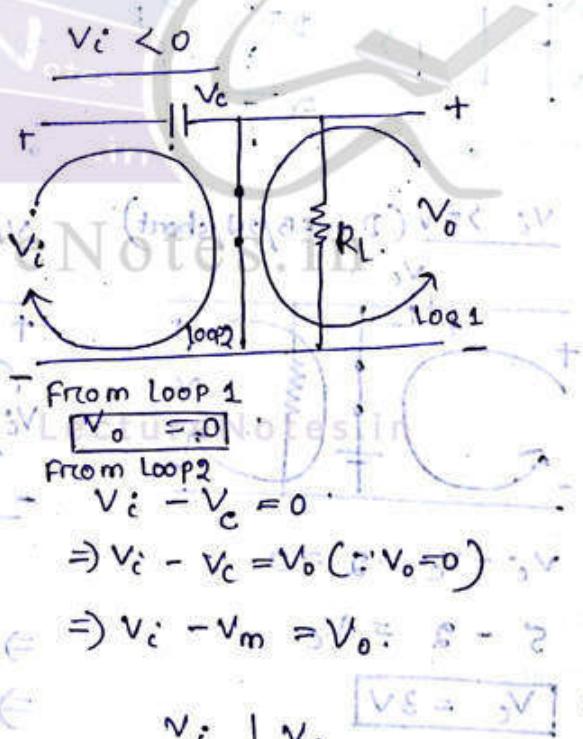

$$From\ Loop\ 1: v_o = 0$$



$$From\ Loop\ 2: v_i - v_c = 0$$

$$\Rightarrow v_i - v_c = v_o (\because v_o = 0)$$


$$\Rightarrow v_i - v_m = v_o$$

$$v_o = v$$


v_i	v_o
0	$-V_m$
V_m	0
$-V_m$	$-2V_m$

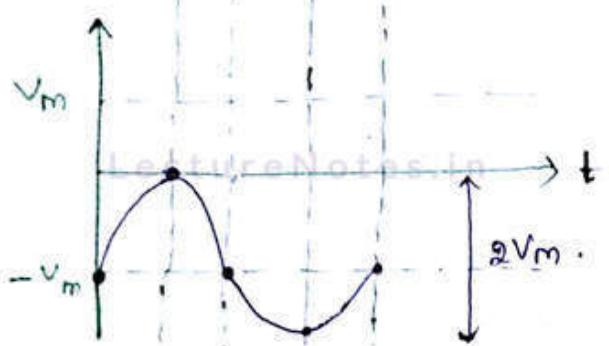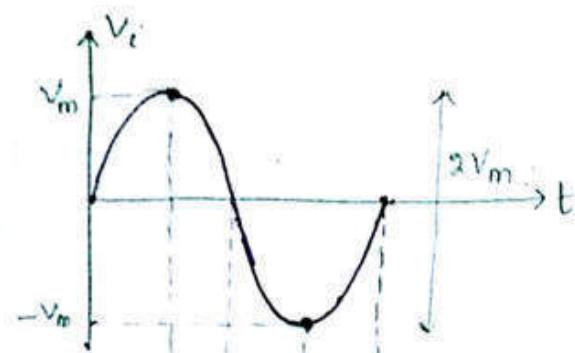

Q.

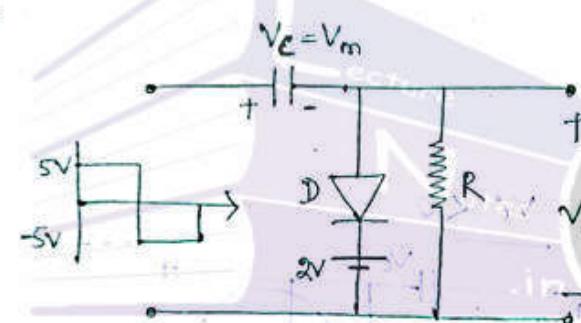

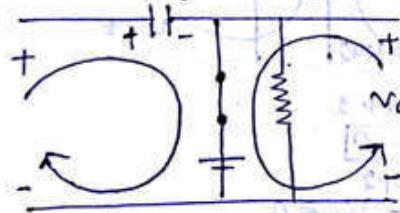
$$\rightarrow \frac{V_i}{2} > 2V \quad (\text{D is FB/ON/short}) \quad \frac{V_i}{2} < 2V \quad (\text{D is RB/OFF/open})$$



$$V_i - V_c - 2V = 0$$

$$\Rightarrow 5 - 2 = V_c$$

$$\Rightarrow V_c = 3V$$


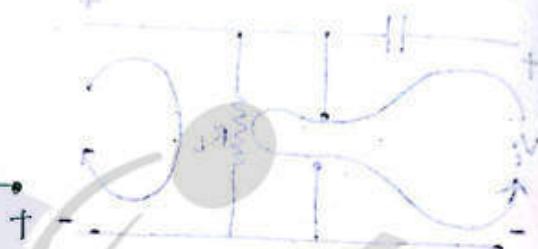


$$V_i - V_c - V_o = 0$$

$$\Rightarrow V_i - V_c = V_o$$

$$\Rightarrow -5 - 3 = V_o$$

$$\Rightarrow V_o = -8V$$

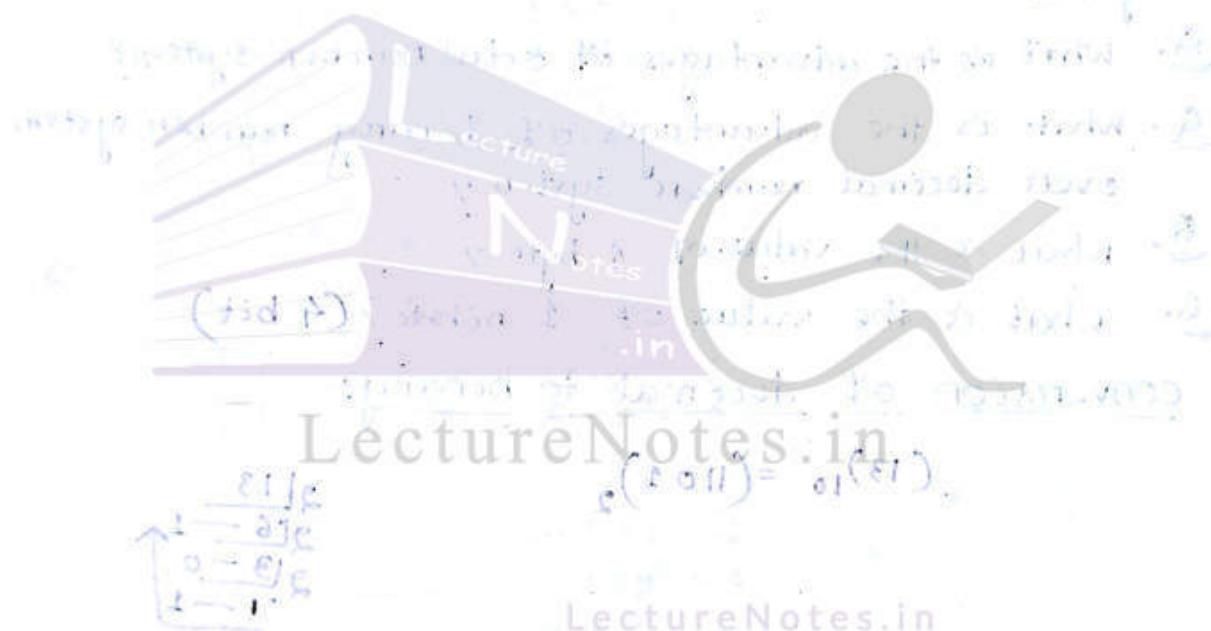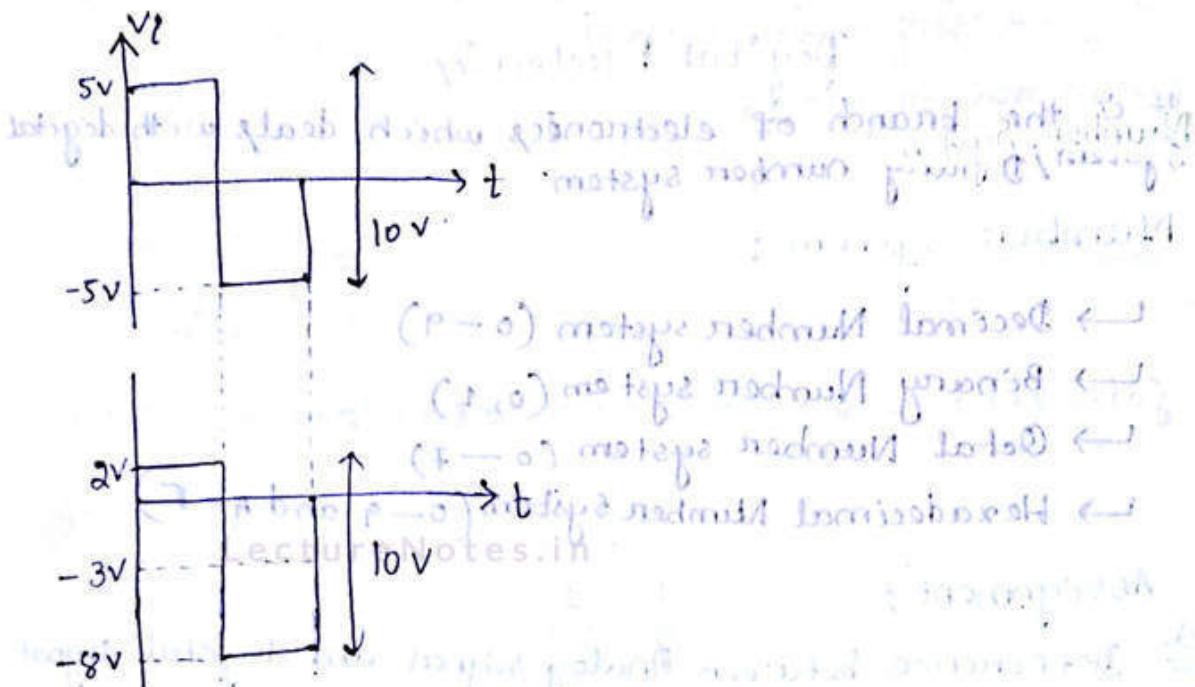

bottom addoh addoh - bottom ←
parasuram & jai matepe nshan bottom left abhi ←
nativib dina matto nshan bottom left nach ston ←
dai war pish nshan bottom left eam ←
geekone - raja dashapad left parrap
- raja parrap as nshan left comath ←
- m hant dant parrap as parrap ←
- raja parrap as parrap as parrap ←
- raja parrap as parrap as parrap ←

$$0.1 \times 2 + 0.1 \times 8 + 0.1 \times 8 = a(2.88)$$



0.1 0.1 0.1

- tipsh fann if nipa fann ← (2)
- tipsh fann if nipa fann ← (2)

Physics of Semiconductor devices:

concept of Diffusion and drift

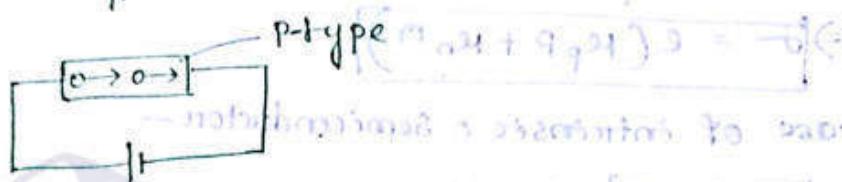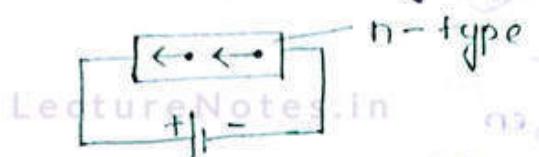- The process of movement of charge carriers due to the concentration gradient is called diffusion and the flow of current due to diffusion is called as diffusion current.
- The process of movement of charge carriers due to application of electric field is called drift and the current flow due to drift is called drift current. The velocity due to drift is called drift velocity.



$$V_d \propto E$$

$$\Rightarrow V_d = kE$$

$$\Rightarrow V_d = k_n E$$

$$\Rightarrow V_d = k_p E$$

$V_d \rightarrow$ drift velocity
 $E \rightarrow$ electric field.
 $k_e \rightarrow$ mobility.
 $k_n \rightarrow$ mobility of e^-
 $k_p \rightarrow$ mobility of holes.

Mobility:

The ability of movement of charge carriers (e^- s and holes) is called mobility.

$$k_e = \frac{V_d}{E}$$

$$\text{Unit of mobility} = \frac{\text{m/s}}{\text{V/m}} = \frac{\text{m/s}}{\text{V/m}} \times \frac{\text{m/V}}{\text{s}} = \text{m}^2/\text{V-s}$$

Conductivity (σ):

- The ability of conduction of charge carriers is called conductivity.
- conductivity is the reciprocal of resistivity.

$$\sigma = \frac{1}{\rho}$$

→ conductivity as the multiplication of concentration, charge and mobility

$$\sigma_p = \mu_e p \quad \text{or} \quad \sigma_p = \mu_h P$$

$$\sigma_n = \mu_e n \quad \text{or} \quad \sigma_n = \mu_h n$$

$p \rightarrow$ concentration of holes
 $n \rightarrow$ concentration of e⁻

$$\sigma_p = \mu_e p eP \quad \text{--- (1)}$$

$$\sigma_n = \mu_h n eN \quad \text{--- (2)}$$

$$\sigma = \sigma_p + \sigma_n$$

$$= \mu_e p eP + \mu_h n eN$$

$$\Rightarrow \sigma = e(\mu_e p + \mu_h n)$$

In case of intrinsic Semiconductors -

$$n_i = p = n_i$$

n_i = intrinsic concentration

$$\sigma = e(\mu_e n_i + \mu_h n_i)$$

$$\sigma = e n_i (\mu_e + \mu_h) \rightarrow \text{conductivity of an intrinsic semiconductor.}$$

Some Important terms related to Semiconductor Physics:

$n \rightarrow$ electron concentration

$p \rightarrow$ hole concentration

$n_i \rightarrow$ intrinsic carrier concentration

$\sigma_n \rightarrow$ conductivity of e⁻

$\sigma_p \rightarrow$ conductivity of holes

$e = q \rightarrow$ electronic charge

$\mu_e \rightarrow$ mobility of e⁻



$\mu_h \rightarrow$ mobility of holes

$N_A \rightarrow$ Acceptor ion concentration

$N_D \rightarrow$ Donor ion concentration

Law of neutrality:

$$n + N_A = p + N_D$$

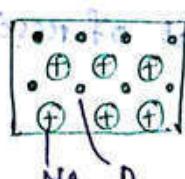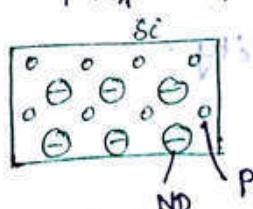

$$\frac{-dV}{dx} = \frac{q}{\epsilon}$$

Note :

for an intrinsic semiconductor

$$n = p = n_i$$

$$n \times p = n_i^2 \quad (\text{mass action law})$$

Mass Action law:

The product of electron concentration and hole concentration is constant at thermal equilibrium. This is called Mass Action law

N-type:

$$N_D = 0$$

$$n \gg p$$

$$n + N_A = p + N_D \quad (n \gg p)$$

$$n + N_A = p$$

P-type:

$$N_A = 0$$

$$p \gg n$$

$$n + N_A = p + N_D \quad (p \gg n)$$

$$p + N_D = n$$

$$\frac{n}{p} \times k_B T \times e^{-\frac{E_F}{k_B T}} = n_i^2$$

N-type:

$$n + N_A = p$$

$$\Rightarrow n_i + N_A = n_i \quad (\because n = p = n_i)$$

$$\Rightarrow N_A = 0$$

$$n + N_A = p + N_D$$

$$\Rightarrow n + 0 = p + N_D \quad (\because n \gg p) \Rightarrow p + N_A = p + 0 \quad (\because p \gg n)$$

$$\Rightarrow n = N_D$$

P-type:

$$p + N_D = n$$

$$\Rightarrow n_i + N_D = n_i \quad (\because n = p = n_i)$$

$$\Rightarrow N_D = 0$$

$$n + N_A = p + N_D$$

$$* n \times p = n_i^2$$

$$\Rightarrow n \times N_A = n_i^2 \quad (\because p = N_A)$$

$$\Rightarrow n = \frac{n_i^2}{N_A}$$

$$\frac{n}{p} \times k_B T \times e^{-\frac{E_F}{k_B T}} = n_i^2$$

$$* n \times p = n_i^2$$

$$\Rightarrow N_D \times p = n_i^2 \quad (\because n = N_D)$$

$$\Rightarrow p = \frac{n_i^2}{N_D}$$

According to the law of neutrality the total concentration of e^- and charge carriers in N-side must be equal to total concentration of hole and the total charge carriers in the P-side.

Current density:

- Current density can be calculated due to the diffusion of holes and due to the diffusion of e^- , and can be represented with J_p and J_n respectively.
- Current density for e^- = the multiplication of charge, diffusion constant for e^- and concentration gradient for e^- .

$$J_n = q \times D_n \times \frac{dn}{dx}$$

D_n = Diffusion constant for e^-

$\frac{dn}{dx}$ = concentration gradient for e^-

- The current density for hole is the product of -ve of charge, concentration gradient of hole and diffusion constant for hole.

$$J_p = -q \times D_p \times \frac{dp}{dx}$$

D_p = diffusion constant for hole.

$\frac{dp}{dx}$ = concentration gradient for hole.

- As the mobility and diffusion are statistical phenomena it is not surprising that they obey Einstein relation

$$\frac{D_n}{k_{\text{B}} n} = \frac{D_p}{k_{\text{B}} p} = \frac{kT}{q}$$

D_n = diffusion constant for e^-

D_p = diffusion constant for hole.

k_{B} = mobility of e^-

$k_{\text{B}} p$ = mobility of hole.

k = Boltzmann constant

T = Temperature

q = charge